

# Combinational Logic

CMPT 295 Week 10.1

# Hardware Design

- Understand how processors work
  - Requires digital systems knowledge
- Understand how code is actually executed on a computer to analyze:
  - Reliability
  - Performance
  - Security
- Layered abstractions
  - Transistors → Combinational Logic → Sequential Logic → Processors → Machine Language → Assembly → High-level Programming Languages → Application programs
  - At each step we can “abstract away” the lower layers

# Synchronous Digital Systems (SDS)

*Hardware of a processor (e.g., RISC-V) is an example of a Synchronous Digital System*

## *Synchronous:*

- All operations coordinated by a central clock
  - “Heartbeat” of the system (processor frequency)

## *Digital:*


- Represent all values with two discrete values
- Electrical signals are treated as 1's and 0's
  - High/Low voltage represent True/False, 1/0

# Moore's Law

- ❖ **Original Version (1965):** Since the integrated circuit was invented, the number of transistors in an integrated circuit has roughly doubled every year; this trend would continue for the foreseeable future
- ❖ 1975: Revised - circuit complexity doubles every two years
 
## Moore's Law – The number of transistors on integrated circuit chips (1971-2018)

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important as other aspects of technological progress – such as processing speed or the price of electronic products – are linked to Moore's law.



Data source: Wikipedia ([https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count))

The data visualization is available at [OurWorldinData.org](https://ourworldindata.org). There you find more visualizations and research on this topic.

Licensed under [CC-BY-SA](#) by the author Max Roser.

# Moore's Law

- ❖ **Original Version (1965):** Since the integrated circuit was invented, the number of transistors in an integrated circuit has roughly doubled every year; this trend would continue for the foreseeable future
- ❖ 1975: Revised - circuit complexity doubles every two years
- ❖ **Hardware Trend:** Hardware gets more powerful every year (due to technology advancement and the hard work of many engineers)
- ❖ **Software Trend:** Software gets faster and uses more resources (And has to keep up with ever-changing hardware)
- ❖ Digital circuits are used to build hardware


# Combinational vs. Sequential Logic

- *Digital Systems* consist of two basic types of circuits:
  - Combinational Logic (CL)
    - Output is a function of the inputs only, not the history of its execution
    - Example: add A, B (ALUs)
  - Sequential Logic (SL)
    - Circuits that “remember” or store information
    - Also called “State Elements”
    - Example: Memory and registers

# Simple Logic Gates

- Special names and symbols:

**NOT**

 


True if input is false

Truth Table

a	NOT a
0	1
1	0


**AND**

 

True if both inputs are true

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1

**OR**

 

True if at least one input is true

a	b	A OR b
0	0	0
0	1	1
1	0	1
1	1	1



# More Simple Logic Gates

Inverted versions are easier to implement in CMOS


**NAND**



True if at least one input is false

a	b	a NAND b
0	0	1
0	1	1
1	0	1
1	1	0


**NOR**

 

True if both inputs are false

a	b	a NOR b
0	0	1
0	1	0
1	0	0
1	1	0


**XOR**

 

True if exactly one input is true

a	b	a XOR b
0	0	0
0	1	1
1	0	1
1	1	0

# Combining Multiple Logic Gates

 

$$D = (\text{NOT}(A \text{ AND } B)) \text{ AND } (A \text{ OR } (\text{NOT } B \text{ AND } C))$$


# How to Represent Combinational Logic?

- ✓ Text Description
- ✓ Circuit Diagram
  - Transistors and wires
  - Logic Gates
- ✓ Truth Table
- ✓ Boolean Expression
- ✓ All are equivalent*

# Truth Tables

- Table that relates the inputs to a combinational logic circuit to its output
  - Output *only* depends on current inputs
  - Use abstraction of 0/1 (F/T) instead of high/low Voltage
  - Shows output for *every* possible combination of inputs
- How big is a truth table with N inputs?
  - 0 or 1 for each of N inputs, so  $2^N$  rows

# N-input Truth Tables

 


A	B	C	Y
0	0	0	F(0,0,0) 0
0	0	1	F(0,0,1) 1
0	1	0	F(0,1,0) 0
0	1	1	F(0,1,1) 0
1	0	0	F(1,0,0) 0
1	0	1	F(1,0,1) 1
1	1	0	F(1,1,0) 1
1	1	1	F(1,1,1) 0

For N inputs, how many distinct functions F do we have?

Function maps each row to 0 or 1, so  $2^{2^N}$  possible functions

# Truth Tables with Multiple Outputs

 

- For 3 outputs, just three indep. functions:  
 $X(A,B,C,D)$ ,  $Y(A,B,C,D)$ , and  $Z(A,B,C,D)$ 
  - Can show functions in separate columns (no additional rows)

**Question:** Which of the columns A-D is the correct output of the Truth Table for:  $(X \text{ XOR } Y) \text{ OR } (\text{NOT } Z)$

X	Y	Z	(A)	(B)	(C)	(D)
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	1	0
1	1	1	1	0	1	1

**Question:** Which of the columns A-D is the correct output of the Truth Table for:  $(X \text{ XOR } Y) \text{ OR } (\text{NOT } Z)$

X	Y	Z	(A)	(B)	(C)	(D)
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	1	0
1	1	1	1	0	1	1




# More Complex Truth Tables

## 3-Input Majority

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

## 2-bit Adder

 

How many  
rows?

A		B		C		
$a_1$	$a_0$	$b_1$	$b_0$	$c_2$	$c_1$	$c_0$
			.			
			.			
			.			

# Truth Tables Don't Scale

- Truth tables are huge
  - Write out EVERY combination of inputs and outputs (thorough, but inefficient)
  - Finding a particular combination of inputs involves scanning a large portion of the table
- Boolean Algebra is a shorter way to represent combinational logic

# Boolean Algebra

- Represent inputs and outputs as variables
  - Each variable can only take on the value 0 or 1
- Overbar or  $\neg$  is NOT: “logical complement”
  - e.g. if A is 0,  $\bar{A}$  is 1. If A is 1, then  $\neg A$  is 0
- Plus (+) is 2-input OR: “logical sum”
- Product ( $\cdot$ ) is 2-input AND: “logical product”
  - Sometimes omitted
- All other gates and logical expressions can be built from combinations of these

$$\bar{A}\bar{B} + A\bar{B} == (\text{NOT}(A \text{ AND } B)) \text{ OR } (A \text{ AND } (\text{NOT } B))$$

# Laws of Boolean Algebra

These laws allow us to simplify Boolean expressions:

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\bar{x}y + x = x + y$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$(\bar{x} + y)x = xy$$

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

complementarity

laws of 0's and 1's

identities

idempotent law

commutativity

associativity

distribution

uniting theorem

uniting theorem v.2

DeMorgan's Law

# Converting Truth Table to Boolean Expression

- Read off of table
  - For 1, write variable name
  - For 0, write complement of variable
- *Sum of Products (SoP)*
  - Take rows with 1's in output column, sum products of inputs
  - $c = \bar{a}b + a\bar{b}$

a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

- *Product of Sums (PoS)*
  - Take rows with 0's in output column, product the sum of the *complements of the inputs*
  - $c = (a + b) \cdot (\bar{a} + \bar{b})$

We can show that these are equivalent!

# Simplifying Boolean Expressions

- **Logic Delay:** Everything we are dealing with is just an abstraction of transistors and wires
  - Inputs propagating to the outputs are voltage signals passing through transistor networks
  - There is always some *delay* before a CL's output updates to reflect the inputs
  - Critical Path is longest delay from any input to output. Could be represented as “n gate delays”
- Simpler Boolean expressions  $\leftrightarrow$  smaller transistor networks  $\leftrightarrow$  smaller circuit delays  $\leftrightarrow$  faster hardware

# Simplifying Boolean Expressions: Example

$$y = ab + a + c$$

# Karnaugh Maps

- Used to simplify Boolean expressions of 2-4 variables
- Table composed of squares each representing a unique combination of all variable (1 if true, else blank)

- Two variable Map:

$xy$	0	1
0	$\bar{x}\bar{y}$	$\bar{x}y$
1	$x\bar{y}$	$xy$

Example: Boolean Expression?

$xy$	0	1
0		1
1	1	1

$$x \neq y$$




# Three Variable Karnaugh Maps

		$yz$		00	01	11	10
$x$	0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}y\bar{z}$	$\bar{x}yz$		
	1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xy\bar{z}$	$xyz$		

Question: Simplify  $\bar{A}C + \bar{A}B + A\bar{B}C + BC$

# Example: Simplify 3-Variable Expression

 Question: Simplify  $\bar{A}C + \bar{A}B + A\bar{B}C + BC$



Answer:  $C + \bar{A}B$


# Four Variable Karnaugh Maps

	$yz$	00	01	11	10	
	$wx$					
00		$\bar{w}\bar{x}\bar{y}\bar{z}$	$\bar{w}\bar{x}\bar{y}z$	$\bar{w}\bar{x}yz$	$\bar{w}\bar{x}y\bar{z}$	
01		$\bar{w}x\bar{y}\bar{z}$	$\bar{w}x\bar{y}z$	$\bar{w}xyz$	$\bar{w}xy\bar{z}$	
11		$wx\bar{y}\bar{z}$	$wx\bar{y}z$	$wxyz$	$wxy\bar{z}$	
10		$w\bar{x}\bar{y}\bar{z}$	$w\bar{x}\bar{y}z$	$w\bar{x}yz$	$w\bar{x}y\bar{z}$	

Question: Simplify  $\bar{w}y + \bar{w}^z\bar{z} + w\bar{x}y + wxyz$
 
# Example: Simplify 4-Variable Expression

Simplify  $\bar{w}y + \bar{w}z + w\bar{x}y + wxyz$




Solution:  $\bar{w}y + \bar{w}z + yz + \bar{x}y$

# Useful Combinational Circuits

 
# Data Multiplexor (MUX)

- Multiplexor (“MUX”) is a *selector*
  - Place one of multiple inputs onto output (N-to-1)
- Shown below is an n-bit 2-to-1 MUX
  - Input S selects between two inputs of n bits each



# Implementing a 1-bit 2-to-1 MUX

- Schematic:**

 


- Truth Table:**

s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Boolean Algebra:**


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

- Circuit Diagram:**

 

# 1-bit 4-to-1 MUX

- Schematic:**

 

- Truth Table:** How many rows?  $2^6$


- Boolean Expression:**

$$E = \overline{S_1}S_0A + \overline{S_1}S_0B + S_1\overline{S_0}C + S_1S_0D$$



 
# Another Design for 4-to-1 MUX

- Can we leverage what we've previously built?
  - Alternative hierarchical approach:



# Full Adder

 


function table:

basically a truth table

A	B	C	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3-bit  
Addition!

 

Full Adder

Q. What's the propagation delay?

3 gate delays (highlighted)

Q. What does the circuit accomplish?

Algebra:  $S = A \oplus B \oplus C$ ;  $C = (A \& B) \mid (C \& (A \oplus B))$

$$S = A \oplus B \oplus C$$