

Combinational Logic

Sequential Logic

CPU Datapath

CMPT 295 Week 10

Synchronous Digital Systems (SDS)

Hardware of a processor (e.g., RISC-V) is an example of a Synchronous Digital System

Synchronous:

- All operations coordinated by a central clock
 - “Heartbeat” of the system (processor frequency)

Digital:


- Represent all values with two discrete values
- Electrical signals are treated as 1's and 0's
 - High/Low voltage represent True/False, 1/0

Moore's Law

- ❖ **Original Version (1965):** Since the integrated circuit was invented, the number of transistors in an integrated circuit has roughly doubled every year; this trend would continue for the foreseeable future
- ❖ 1975: Revised - circuit complexity doubles every two years
- ❖ **Hardware Trend:** Hardware gets more powerful every year (due to technology advancement and the hard work of many engineers)
- ❖ **Software Trend:** Software gets faster and uses more resources (And has to keep up with ever-changing hardware)
- ❖ Digital circuits are used to build hardware


Transistors to Gates Example: Inverter

 - ❖ CMOS technology
- ❖ Two transistors:
 - NMOS (top): turns on when input is 0 (low V)
 - PMOS (bottom): turns on when input is 1 (high V)




Transistors to Gates Example: Inverter

 - ❖ Input = 0
- ❖ Top transistor turned on, bottom transistor turned off -> Output connected to VDD, capacitor charged
- ❖ Output = 1



Transistors to Gates Example: Inverter

 - ❖ Input = 1
- ❖ Top transistor turned off, bottom transistor turned on -> Output connected to GND, capacitor discharged
- ❖ Output = 0



Inverter is commonly called “NOT gate”


Combinational vs. Sequential Logic

- *Digital Systems* consist of two basic types of circuits:
 - Combinational Logic (CL)
 - Output is a function of the inputs only, not the history of its execution
 - Example: add A, B (ALUs)
 - Sequential Logic (SL)
 - Circuits that “remember” or store information
 - Also called “State Elements”
 - Example: Memory and registers

Simple Logic Gates

- Special names and symbols:

NOT

 


True if input is false

Truth Table

a	NOT a
0	1
1	0


AND

 

True if both inputs are true

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

True if at least one input is true

a	b	A OR b
0	0	0
0	1	1
1	0	1
1	1	1

More Simple Logic Gates

Inverted versions are easier to implement in CMOS


NAND



True if at least one input is false

a	b	a NAND b
0	0	1
0	1	1
1	0	1
1	1	0


NOR

 

True if both inputs are false

a	b	a NOR b
0	0	1
0	1	0
1	0	0
1	1	0


XOR

 

True if exactly one input is true
(or if odd number of inputs are true for > 2 inputs)

a	b	a XOR b
0	0	0
0	1	1
1	0	1
1	1	0

Combining Multiple Logic Gates

 

$$D = (\text{NOT}(\mathbf{A \text{ AND } B})) \text{ AND } (\mathbf{A \text{ OR } (NOT B \text{ AND } C)})$$


How to Represent Combinational Logic?

- ✓ Text Description
- ✓ Circuit Diagram
 - Transistors and wires
 - Logic Gates
- ✓ Truth Table
- ✓ Boolean Expression
- ✓ All are equivalent*

Useful Combinational Circuits


Data Multiplexor (MUX)

 - Multiplexor (“MUX”) is a *selector*
 - Place one of multiple inputs onto output (N-to-1)
- Shown below is an n-bit 2-to-1 MUX
 - Input S selects between two inputs of n bits each



Implementing a 1-bit 2-to-1 MUX

- Schematic:**

 

- Truth Table:**


s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

	AB	00	01	11	10
s = 0				1	1
s = 1			1	1	

- Boolean Algebra:**


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

- Circuit Diagram:**

 

1-bit 4-to-1 MUX

- Schematic:**

 


- Truth Table:** How many rows? 2^6

- Boolean Expression:**

$$E = \overline{S_1} \overline{S_0} A + \overline{S_1} S_0 B + S_1 \overline{S_0} C + S_1 S_0 D$$


Another Design for 4-to-1 MUX

 - Can we leverage what we've previously built?
 - Alternative hierarchical approach:



Decoder

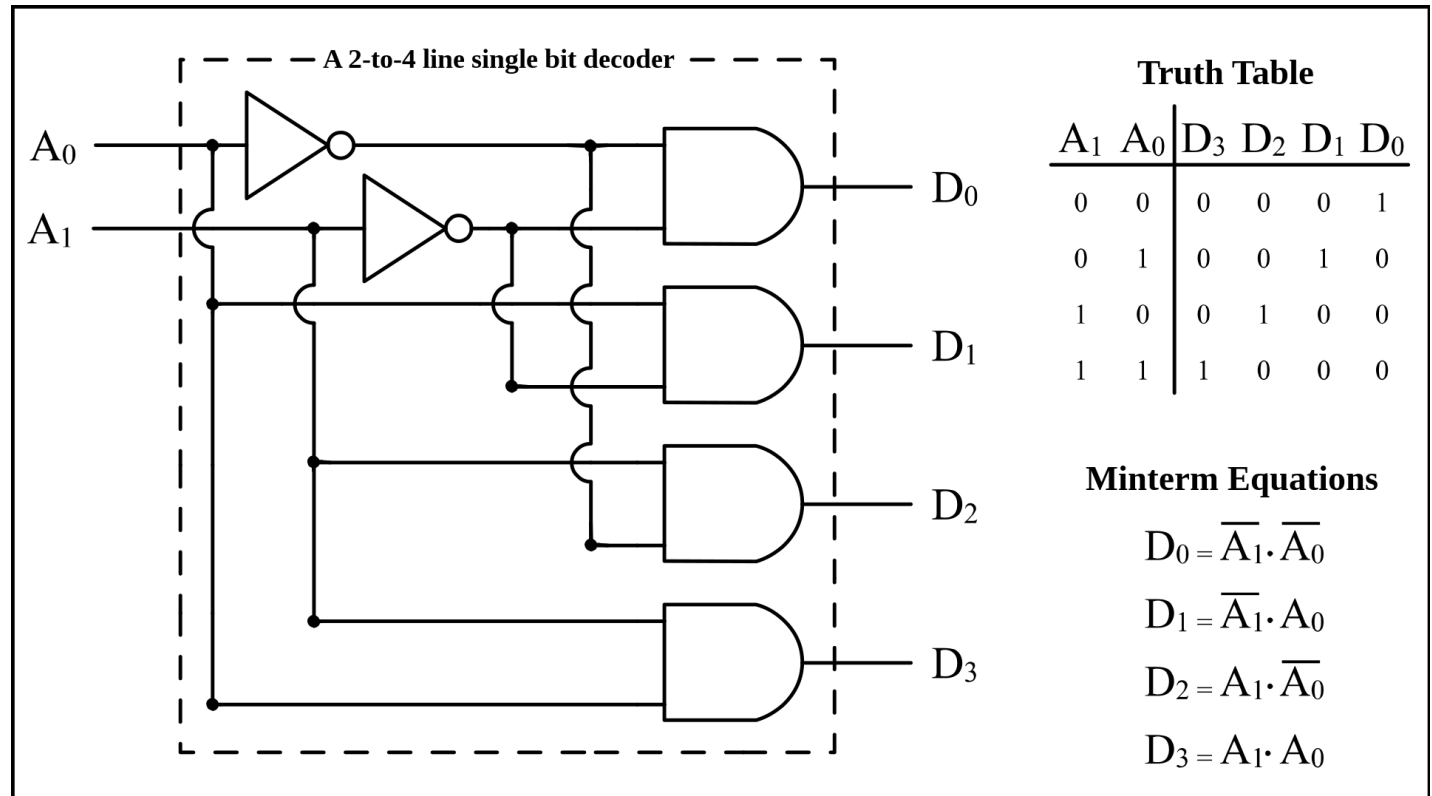- Enable one of 2^N outputs based on N input
- Example: 2-to-4 decoder




By BlueJester0101, CC BY-SA 3.0, <https://commons.wikimedia.org/w/index.php?curid=3668293>

- Use case: Choose ALU operation based on instruction op-code

Demultiplexer (Demux)

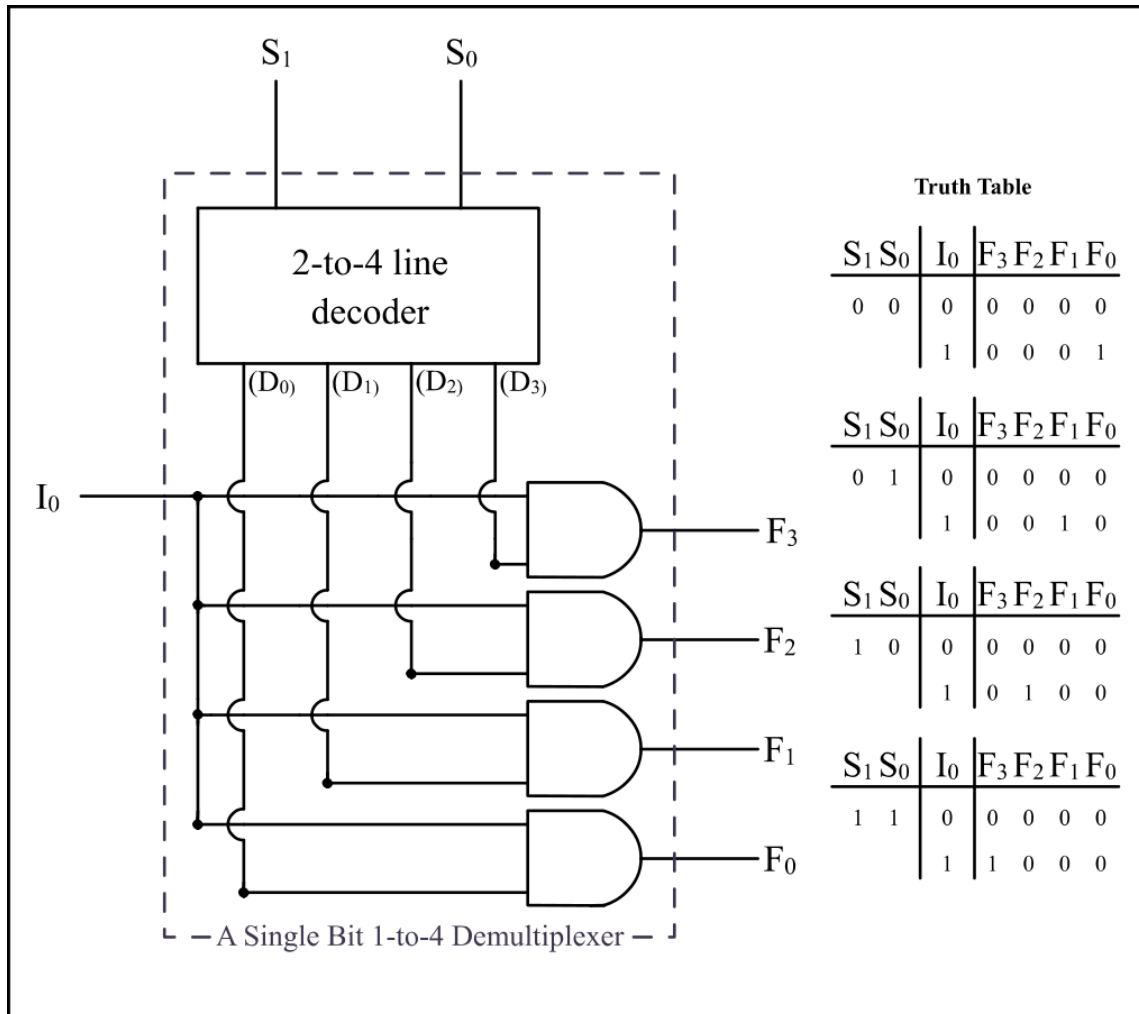- Similar to decoder with an enable signal




By BlueJester0101, CC BY-SA 3.0,
<https://commons.wikimedia.org/w/index.php?curid=3668293>

Single-Bit Binary Adder (Half Adder)


- Add $A + B$ to get Sum (S) and Carry (C)
- Truth Table:
- Boolean Expressions:
 - $S = A \oplus B$; $C = AB$
- Circuit:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

By inductiveload - Own work, Public Domain,
<https://commons.wikimedia.org/w/index.php?curid=1023090>


What is this Circuit?

 

Truth table:

A	B	C	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
<hr/>				
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3-bit
Addition!

 

Q. What's the propagation delay?

➤ 3 gate delays (highlighted)

Full Adder

Q. What does the circuit accomplish?


➤ Algebra:

$$S = A \oplus B \oplus C ; C = AB + C(A \oplus B)$$

Computing with Combinational Circuits

Definition: A combinational circuit computes a pure function, i.e., its outputs react only based on its inputs. There are no feedback loops and no state information (memory) is maintained.

 Theorem: Every Boolean function can be implemented with NAND and NOT. Circuits are modular




... a 4-bit ripple carry adder!

- Adds by columns
- Propagation delay

= 9

$$(2n + 1)$$

 


Functional Unit

Hardware circuits are fixed

- Can't adjust wires / gates while running
- Build control wires to parametrize its function


Function Unit:

 

Function Select:

FS	func
0001	$A + B$
0010	$A - B$
1000	$A * B$
0100	$A \wedge B$
0101	$A + 1$
1101	B

Functional Unit: Adder-Subtractor

 

- if $FS == 0$ then
 $S = A + B$
- if $FS == 1$ then
 $S = A + \bar{B} + 1$
 $= A - B$

Combinational vs. Sequential Logic

- *Digital Systems* consist of two basic types of circuits:
 - Combinational Logic (CL)
 - Output is a function of the inputs only, not the history of its execution
 - Example: add A, B (ALUs)
 - Sequential Logic (SL)
 - Circuits that “remember” or store information
 - Also called “State Elements”
 - Example: Memory and registers

Sequential Logic

Accumulator Example

An example of why we would need sequential logic




Want: $S=0;$
for X_1, X_2, X_3 over time...
 $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle
- The sum since time 1 (cycle) is present on S


First Try: Does this work?

 

No!


- 1) How to control the next iteration of the 'for' loop?
- 2) How do we say: ' $S=0$ '?

Second Try: How About This?

 


A *Register* is the state element that is used here to hold up the transfer of data to the adder

Accumulator Revisited: Proper Timing

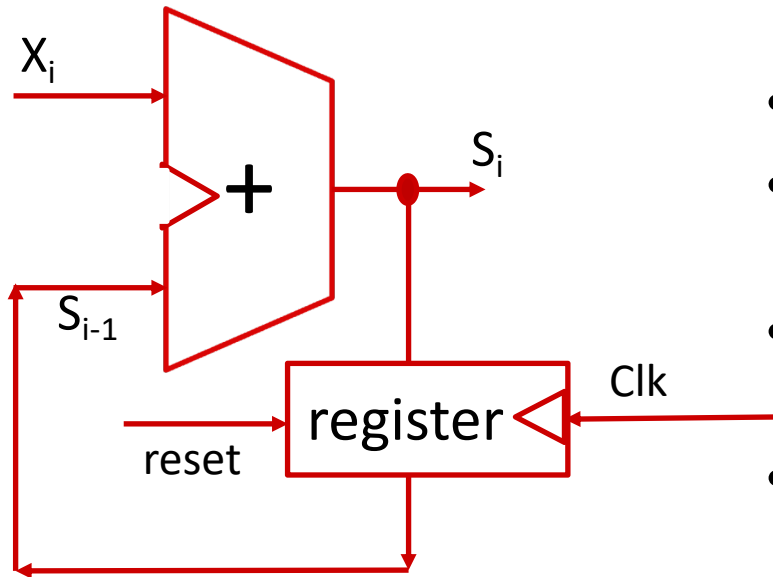

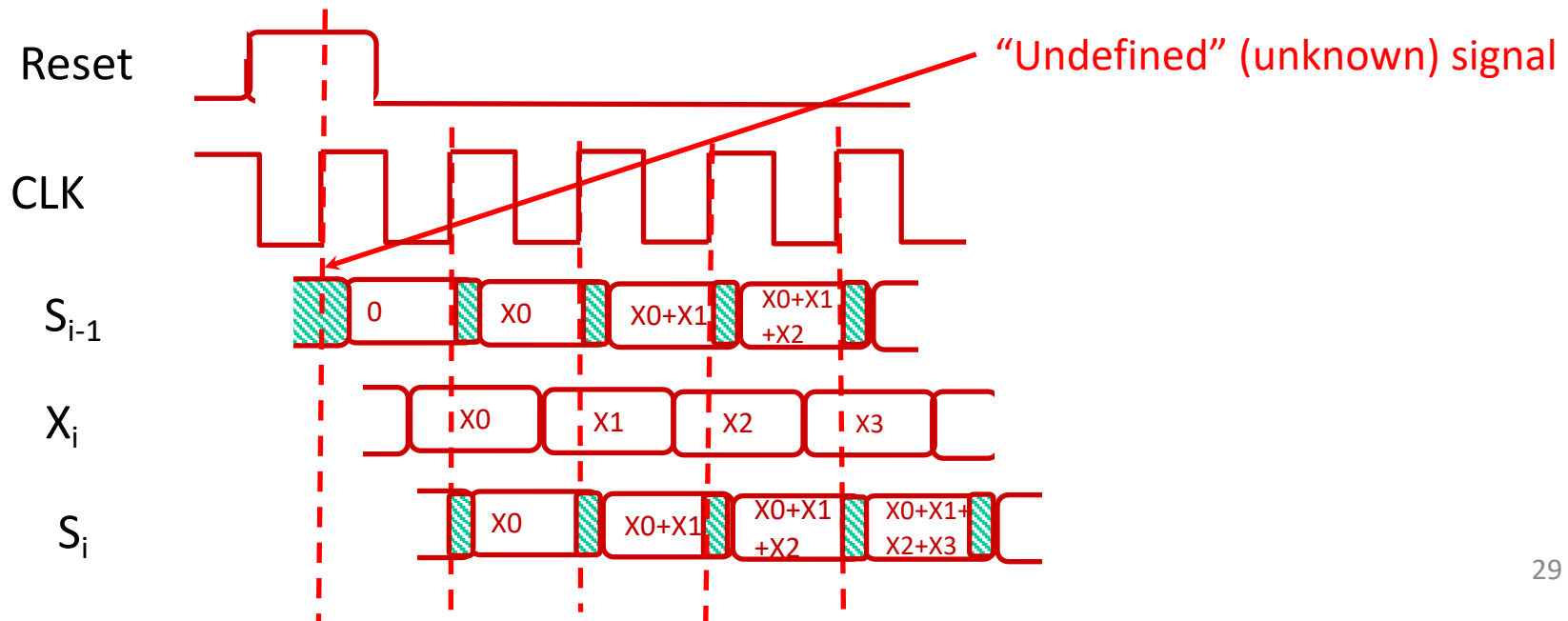- Reset signal shown
- In practice X_i might not arrive to the adder at the same time as S_{i-1}
- S_i temporarily is wrong, but register always captures correct value
- In good circuits, instability never happens around rising edge of CLK



Uses for State Elements

- Place to store values for some amount of time:
 - Register files (like in RISC-V)
 - Memory (caches and main memory)
- *Help control flow of information between combinational logic blocks*
 - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage

CPU Hardware

Goal: Given an instruction set architecture, construct a machine that reliably executes instructions.

Design choices will influence speed of instructions:

- some instructions will be faster than others
- order of instructions may matter
- order of memory accesses may matter


— “conflicts” or “hazards”



Maximum Clock Frequency

- What is the max frequency of this circuit?
 - Limited by how much time needed to get correct Next State to Register (t_{setup} constraint)

Assumes Max Delay > Hold Time

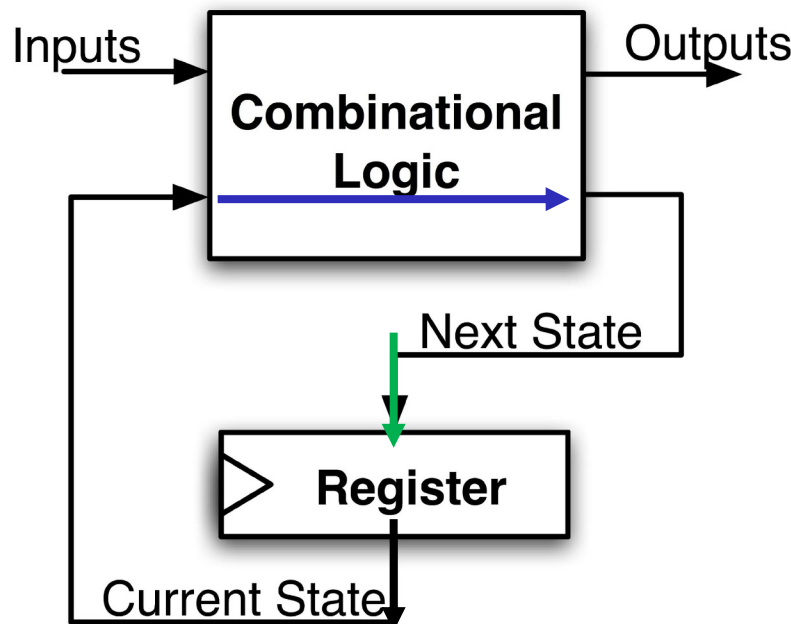


$$\begin{aligned} \text{Max Delay} &= \text{CLK-to-Q Delay} \\ &+ \text{CL Delay} \\ &+ \text{Setup Time} \end{aligned}$$

$$\begin{aligned} \text{Min Period} &= \text{Max Delay} \\ \text{Max Freq} &= 1/\text{Min Period} \end{aligned}$$

The Critical Path

 - The *critical path* is the longest delay between *any* two registers in a circuit
- The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register



How do we go faster?

Pipelining!


- Split operation into smaller parts and add a register between each one.

RISC-V *CPU Datapath, Control Intro*

Design Principles

- Five steps to design a processor:

 - 1) Analyze instruction set → datapath requirements
- 2) Select set of datapath components & establish clock methodology
- 3) Assemble datapath meeting the requirements
- 4) Analyze implementation of each instruction to determine setting of control points that effects the register transfer
- 5) Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits



Summary !

- Universal datapath
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
- 5 Phases of execution
 - IF (Instruction Fetch), ID (Instruction Decode), EX (Execute), MEM (Memory), WB (Write Back)
 - Not all instructions are active in all phases (except for loads!)
- Controller specifies how to execute instructions
 - Worth thinking about: what new instructions can be added with just most control?

Your CPU in two parts


- **Central Processing Unit (CPU):**
 - **Datapath:** contains the hardware necessary to perform operations required by the processor
 - Reacts to what the controller tells it! (ie. “I was told to do an add, so I’ll feed these arguments through an adder)
 - **Control:** decides what each piece of the datapath should do
 - What operation am I performing? Do I need to get info from memory? Should I write to a register? Which register?
 - Has to make decisions based on the input instruction only!

Design Principles


- Determining control signals
 - Any time a datapath element has an input that changes behavior, it requires a control signal (e.g. ALU operation, read/write)
 - Any time you need to pass a different input based on the instruction, add a **MUX** with a control signal as the selector (e.g. next PC, ALU input, register to write to)
- Your control signals will change based on your exact datapath
- Your datapath will change based on your ISA

Storage Element: Register File

- **Register File** consists of 31 registers:
 - Output ports **portA** and **portB**
 - Input port **portW**
- Register selection
 - Place data of register **RA** (number) onto **portA**
 - Place data of register **RB** (number) onto **portB**
 - Store data on **portW** into register **RW** (number) when Write Enable is 1
- Clock input (CLK)
 - CLK is passed to all internal registers so they can be written to if they match **RW** and Write Enable is 1

 

Implementing R-Types

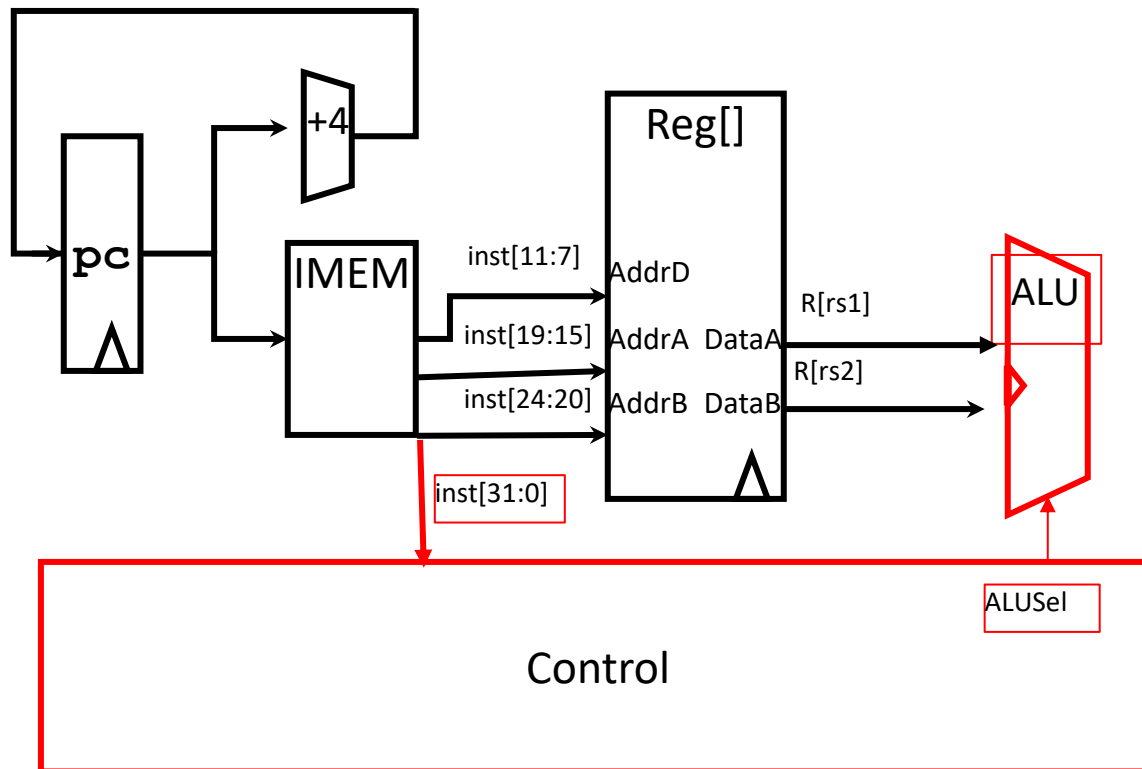


(4) Perform operation

- New hardware: ALU (Arithmetic Logic Unit)
- Abstraction for adders, multipliers, dividers, etc.
- How do we know what operation to execute?
 - Our first control bit! **ALUSel(ect)**


Inst[31:0]	PCSel	ImmSel	RegWEn	Br Un	Br Eq	Br LT	BSel	ASel	ALUSe l	MemRW	WBSel
add	+4	*	1 (Y)	*	*	*	Reg	Reg	Add	Read	ALU
sub	+4	*	1	*	*	*	Reg	Reg	Sub	Read	ALU
(R-R Op)	+4	*	1	*	*	*	Reg	Reg	(Op)	Read	ALU

Adding addi to datapath

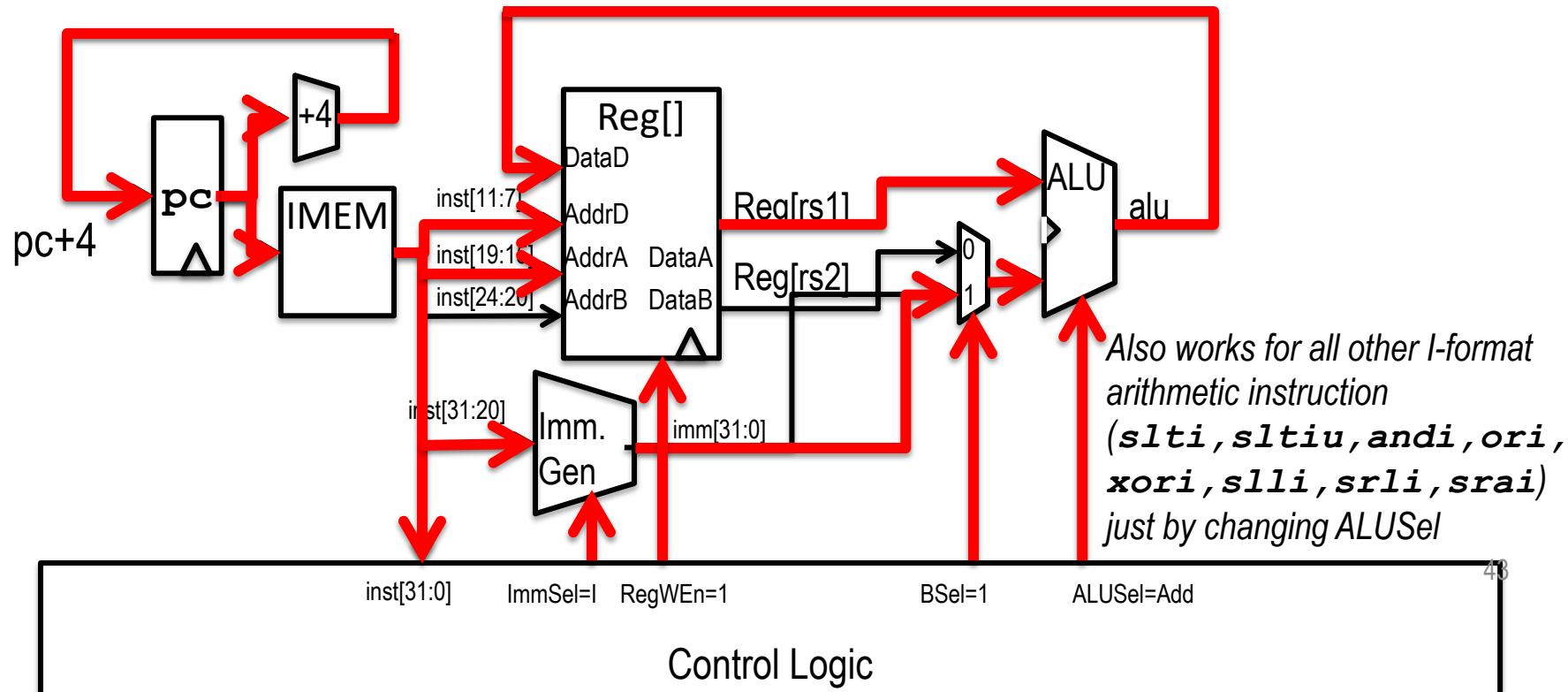

Inst[31:0]	PCSel	ImmSel	RegWEn	Br Un	Br Eq	Br LT	BSel	ASel	ALUSe l	MemRW	WBSel
add	+4	*	1 (Y)	*	*	*	Reg	Reg	Add	Read	ALU
sub	+4	*	1	*	*	*	Reg	Reg	Sub	Read	ALU
(R-R Op)	+4	*	1	*	*	*	Reg	Reg	(Op)	Read	ALU
addi	+4	I	1	*	*	*	Imm	Reg	Add	Read	ALU


Adding lw to datapath

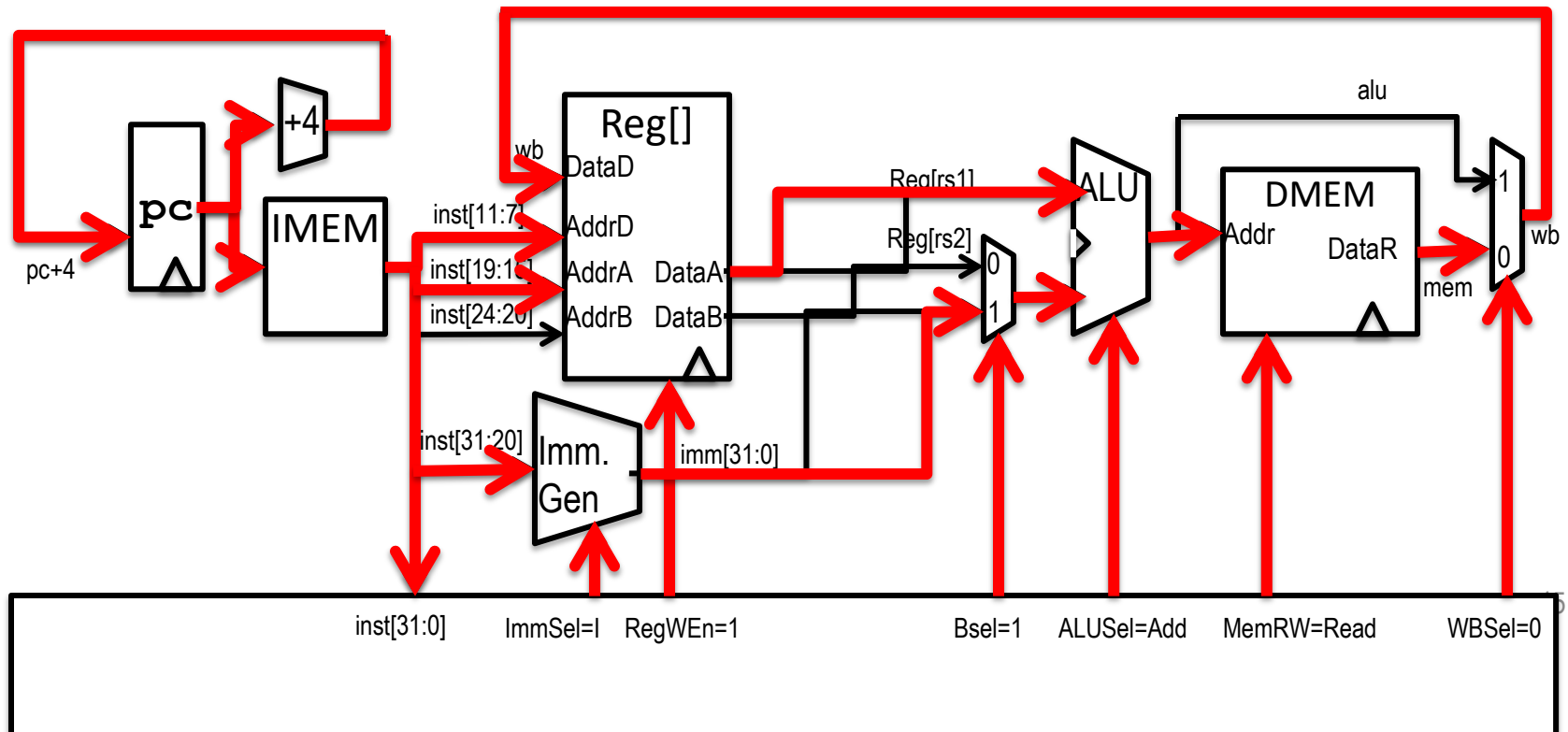


Inst[31:0]	PCSel	ImmSel	RegWEn	Br Un	Br Eq	Br LT	BSel	ASel	ALUSe l	MemRW	WBSel
add	+4	*	1 (Y)	*	*	*	Reg	Reg	Add	Read	ALU
sub	+4	*	1	*	*	*	Reg	Reg	Sub	Read	ALU
(R-R Op)	+4	*	1	*	*	*	Reg	Reg	(Op)	Read	ALU
addi	+4	I	1	*	*	*	Imm	Reg	Add	Read	ALU
lw	+4	I	1	*	*	*	Imm	Reg	Add	Read	Mem

Storage Element: Idealized Memory


- Memory (idealized)
 - One input port: Data In
 - One output port: **Data Out**
- Memory access:
 - Read: Write Enable = 0, data at Address is placed on **Data Out**
 - Write: Write Enable = 1, Data In written to Address
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read, behaves as a combinational logic block: Address valid → **Data Out** valid after “access time”

 

Current Datapath

 


Adding sw to datapath

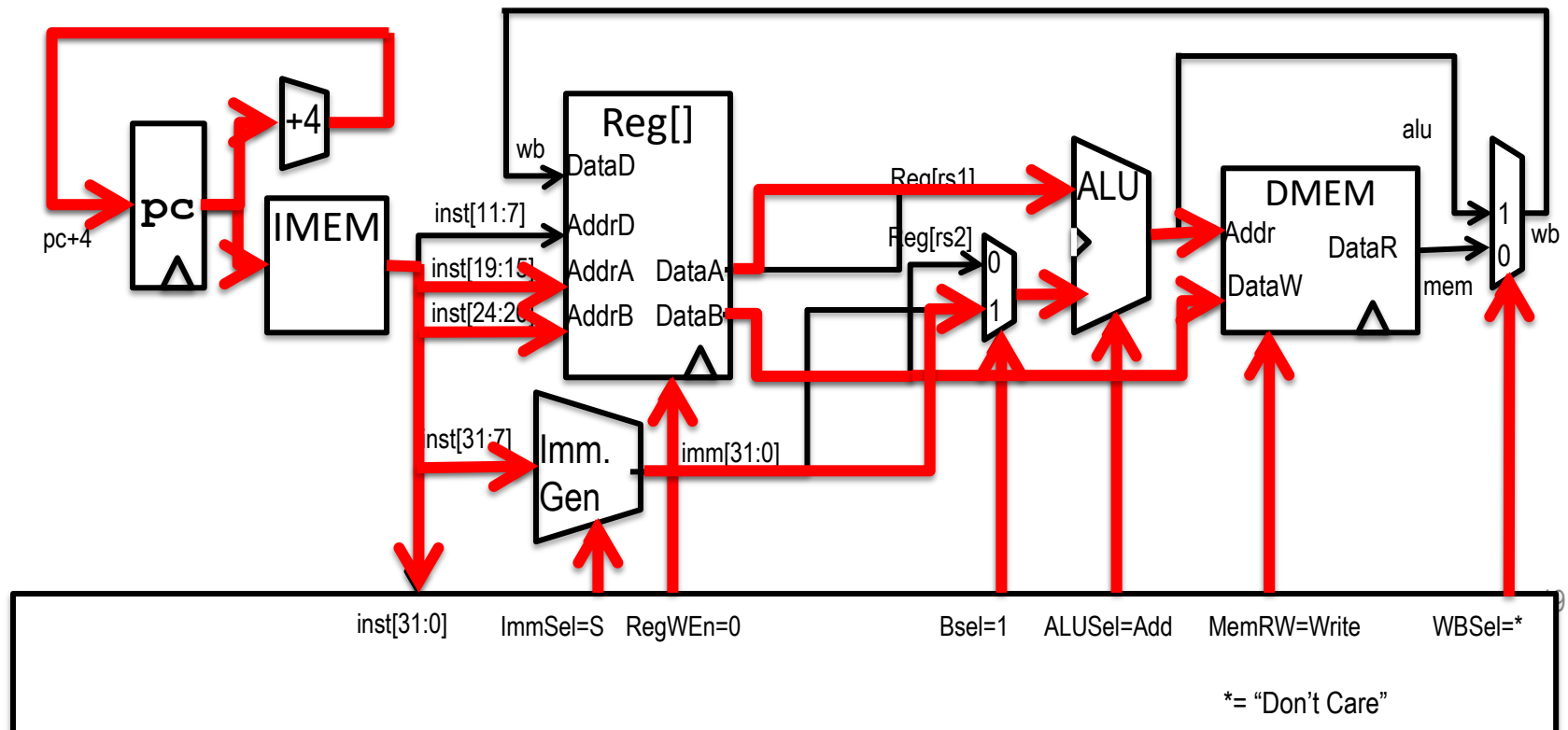


Inst[31:0]	PCSel	ImmSel	RegWEn	Br Un	Br Eq	Br LT	BSel	ASel	ALUSe l	MemRW	WBSel
add	+4	*	1 (Y)	*	*	*	Reg	Reg	Add	Read	ALU
sub	+4	*	1	*	*	*	Reg	Reg	Sub	Read	ALU
(R-R Op)	+4	*	1	*	*	*	Reg	Reg	(Op)	Read	ALU
addi	+4	I	1	*	*	*	Imm	Reg	Add	Read	ALU
lw	+4	I	1	*	*	*	Imm	Reg	Add	Read	Mem
sw	+4	S	0 (N)	*	*	*	Imm	Reg	Add	Write	*

Inst[31:0]	PCSel	ImmSel	RegWEn	Br Un	Br Eq	Br LT	BSel	ASel	ALUSe l	MemRW	WBSel
add	+4	*	1 (Y)	*	*	*	Reg	Reg	Add	Read	ALU
sub	+4	*	1	*	*	*	Reg	Reg	Sub	Read	ALU
(R-R Op)	+4	*	1	*	*	*	Reg	Reg	(Op)	Read	ALU
addi	+4	I	1	*	*	*	Imm	Reg	Add	Read	ALU
lw	+4	I	1	*	*	*	Imm	Reg	Add	Read	Mem
sw	+4	S	0 (N)	*	*	*	Imm	Reg	Add	Write	*
beq	+4	B	0	*	0	*	Imm	PC	Add	Read	*
beq	ALU	B	0	*	1	*	Imm	PC	Add	Read	*
bne	ALU	B	0	*	0	*	Imm	PC	Add	Read	*
bne	+4	B	0	*	1	*	Imm	PC	Add	Read	*
blt	ALU	B	0	0	*	1	Imm	PC	Add	Read	*
bltu	ALU	B	0	1	*	1	Imm	PC	Add	Read	*
jalr	ALU	I	1	*	*	*	Imm	Reg	Add	Read	PC+4
jal	ALU	J	1	*	*	*	Imm	PC	Add	Read	PC+4
auipc	+4	U	1	*	*	*	Imm	PC	Add	Read	ALU


Adding branches to datapath

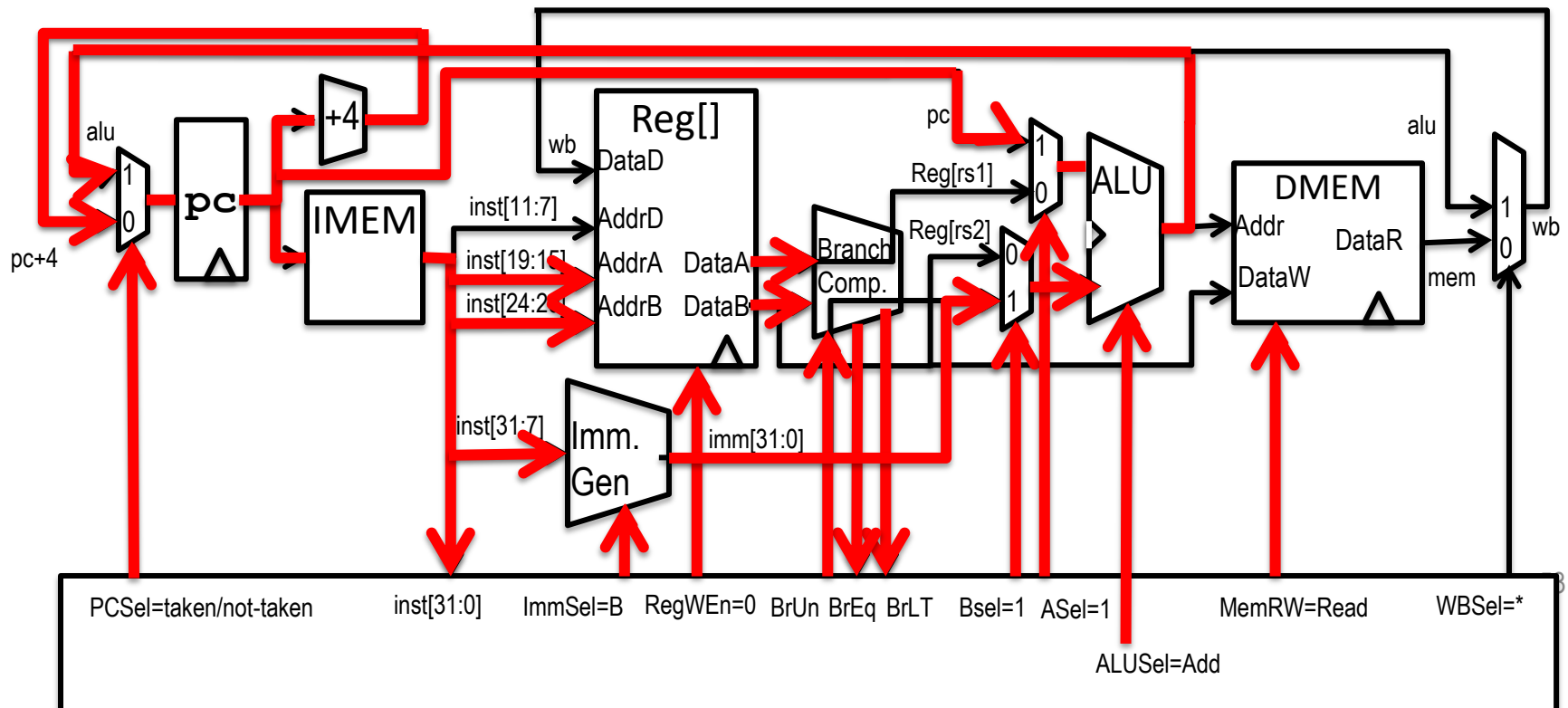


Adding jalr to datapath

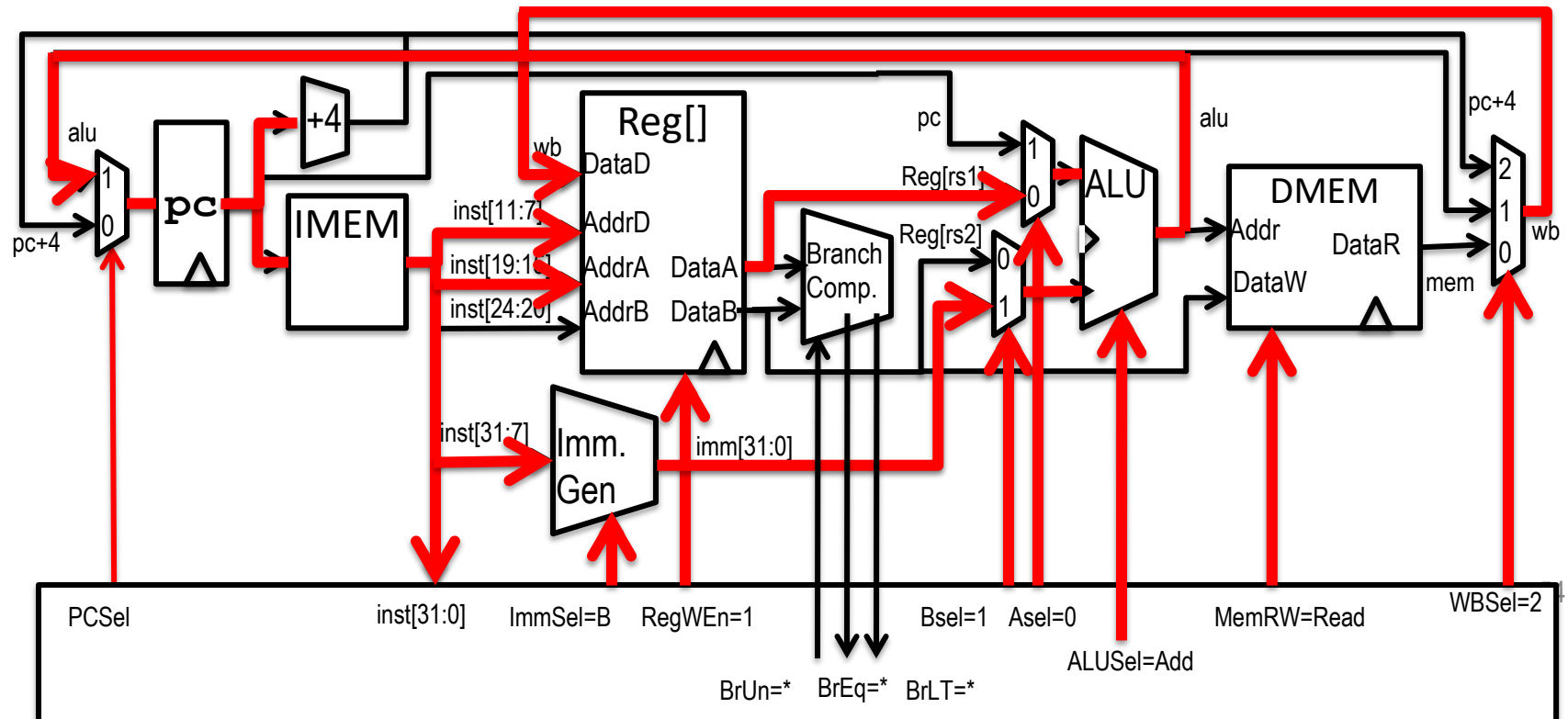

Adding jal to datapath

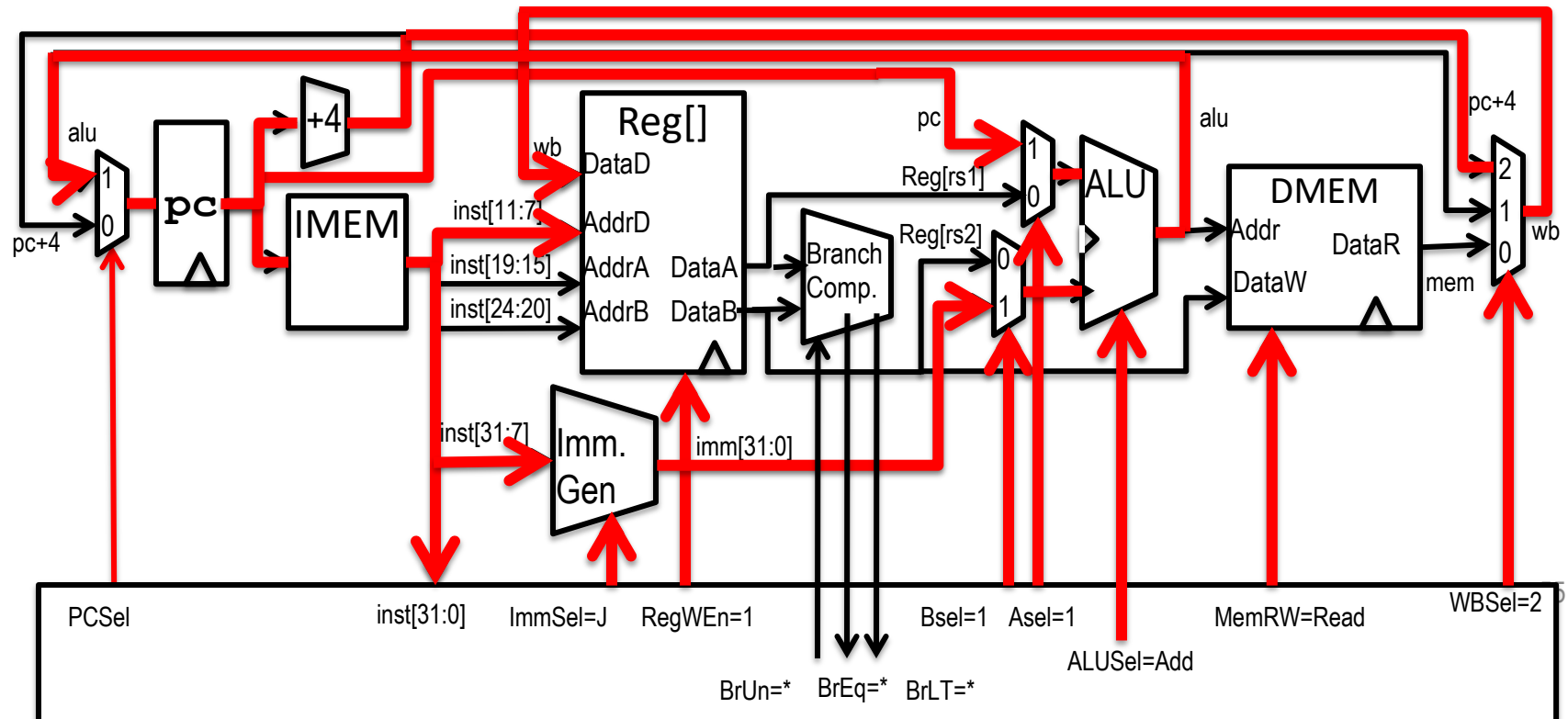

Implementing lui

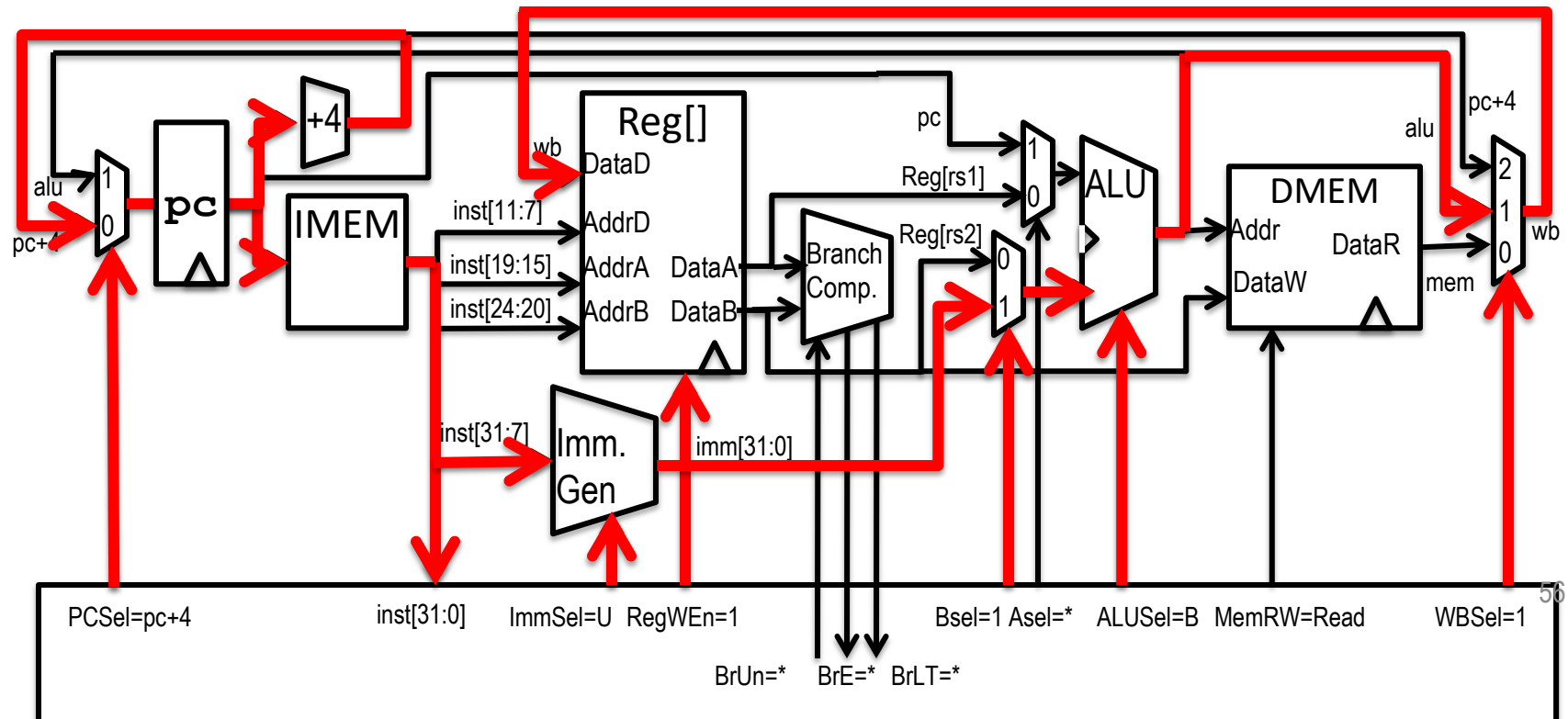

Implementing auipc

