 


Black Box Architecture


A black box is employed to abstract the function of a device.

Notation:

- values of 0 / 1 travel along wires (lines)
- arrows indicate direction of travel
- there are inputs and outputs




Also:

 

After a change in inputs, there is a time delay for outputs

- on a picosecond to nanosecond scale =: propagation delay (t_{pd})
- find longest distance from inputs to outputs

Mystery Circuit : Full Adder

 


function table:

- basically a truth table

A	B	C	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3-bit
Addition!

 

Full Adder

Q. What's the propagation delay?

- 3 gate delays (highlighted)

Q. What does the circuit accomplish?


- algebra: $S = A \oplus B \oplus C$; $C = (A \& B) \mid (C \& (A \oplus B))$

$$S = A \oplus B \oplus C$$

Computing with Combinational Circuits

Definition: A combinational circuit computes a pure function, i.e., its outputs react only based on its inputs. There are no feedback loops and no state information (memory) is maintained.

 Theorem: Every Boolean function can be implemented with NAND and NOT. Circuits are modular




... a 4-bit ripple carry adder!

- adds by columns
- propagation delay

= 9

$$(2n + 1)$$

 


Function Unit

Hardware circuits are fixed

- ⇒ can't adjust wires / gates while running
- ⇒ build control wires to parametrize its function


Function Unit:

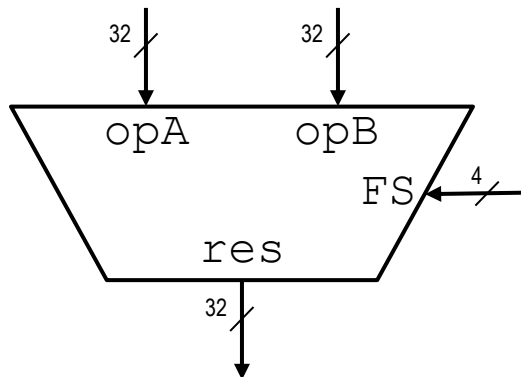

Function Select:

FS	func
0001	A + B
0010	A - B
1000	A * B
0100	A ^ B
0101	A + 1
1101	B


Function Unit: Adder-Subtractor

 

- if $FS == 0$ then
 $S = A + B$
- if $FS == 1$ then
 $S = A + \overline{B} + 1$
 $= A - B$

Digital State Machines

Memory holds state information

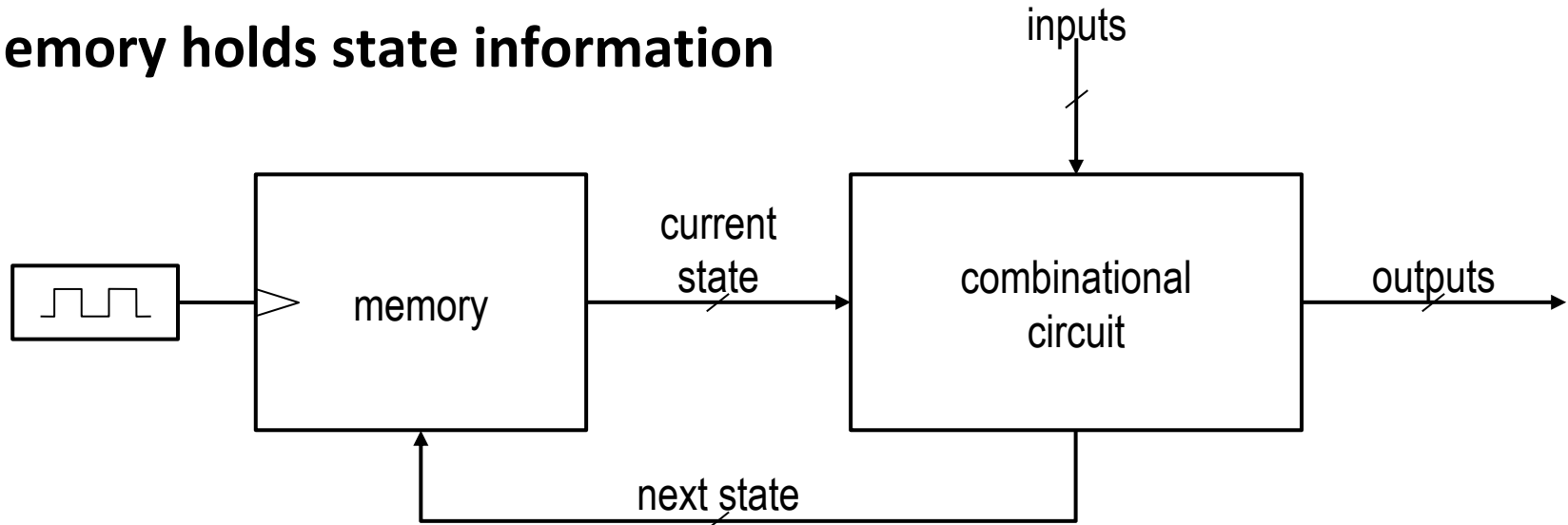

- compute next state based on (current state, inputs)
- compute outputs based on (current state, inputs)

Q. What does this imply about the clock period?

- clock period must exceed (t_{pd} of combinational circuit + t_{pd} of registers)

CPU Hardware

Goal: Given an instruction set architecture, construct a machine that reliably executes instructions.

Design choices will influence speed of instructions:

- **some instructions will be faster than others**
- **order of instructions may matter**
- **order of memory accesses may matter**


— “conflicts” or “hazards”



Maximum Clock Frequency

- What is the max frequency of this circuit?
 - Limited by how much time needed to get correct Next State to Register (t_{setup} constraint)

Assumes Max Delay > Hold Time

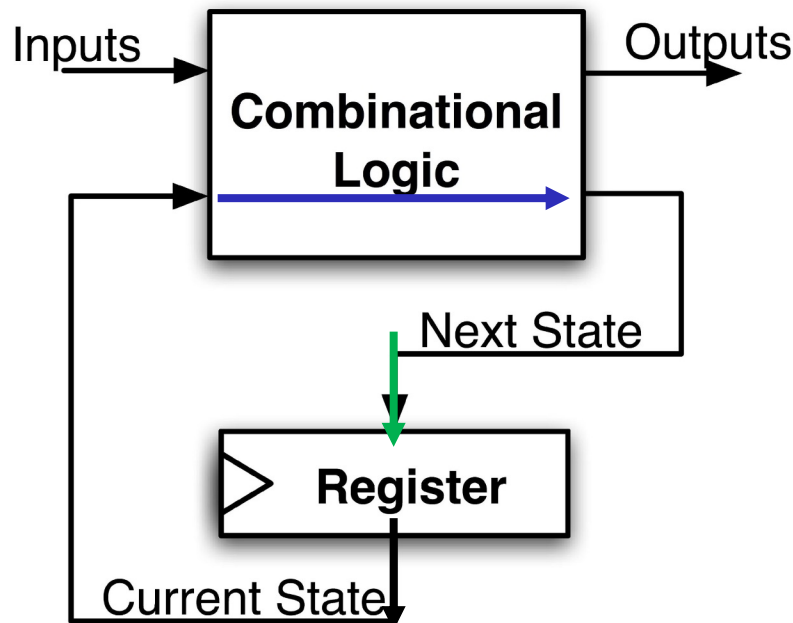


$$\begin{aligned} \text{Max Delay} &= \text{CLK-to-Q Delay} \\ &+ \text{CL Delay} \\ &+ \text{Setup Time} \end{aligned}$$

$$\begin{aligned} \text{Min Period} &= \text{Max Delay} \\ \text{Max Freq} &= 1/\text{Min Period} \end{aligned}$$

The Critical Path

 - The *critical path* is the longest delay between *any* two registers in a circuit
- The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register



How do we go faster?

Pipelining!


- Split operation into smaller parts and add a register between each one.

RISC-V *CPU Datapath, Control Intro*

Design Principles

- Five steps to design a processor:

 - 1) Analyze instruction set → datapath requirements
- 2) Select set of datapath components & establish clock methodology
- 3) Assemble datapath meeting the requirements
- 4) Analyze implementation of each instruction to determine setting of control points that effects the register transfer
- 5) Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits



Summary !

- Universal datapath
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
- 5 Phases of execution
 - IF (Instruction Fetch), ID (Instruction Decode), EX (Execute), MEM (Memory), WB (Write Back)
 - Not all instructions are active in all phases (except for loads!)
- Controller specifies how to execute instructions
 - Worth thinking about: what new instructions can be added with just most control?

Your CPU in two parts


- **Central Processing Unit (CPU):**
 - **Datapath:** contains the hardware necessary to perform operations required by the processor
 - Reacts to what the controller tells it! (ie. “I was told to do an add, so I’ll feed these arguments through an adder)
 - **Control:** decides what each piece of the datapath should do
 - What operation am I performing? Do I need to get info from memory? Should I write to a register? Which register?
 - Has to make decisions based on the input instruction only!

Design Principles


- Determining control signals
 - Any time a datapath element has an input that changes behavior, it requires a control signal (e.g. ALU operation, read/write)
 - Any time you need to pass a different input based on the instruction, add a **MUX** with a control signal as the selector (e.g. next PC, ALU input, register to write to)
- Your control signals will change based on your exact datapath
- Your datapath will change based on your ISA

Storage Element: Register File

- **Register File** consists of 31 registers:
 - Output ports **portA** and **portB**
 - Input port **portW**
- Register selection
 - Place data of register **RA** (number) onto **portA**
 - Place data of register **RB** (number) onto **portB**
 - Store data on **portW** into register **RW** (number) when **Write Enable** is 1
- Clock input (CLK)
 - CLK is passed to all internal registers so they can be written to if they match **RW** and **Write Enable** is 1

 


Implementing R-Types

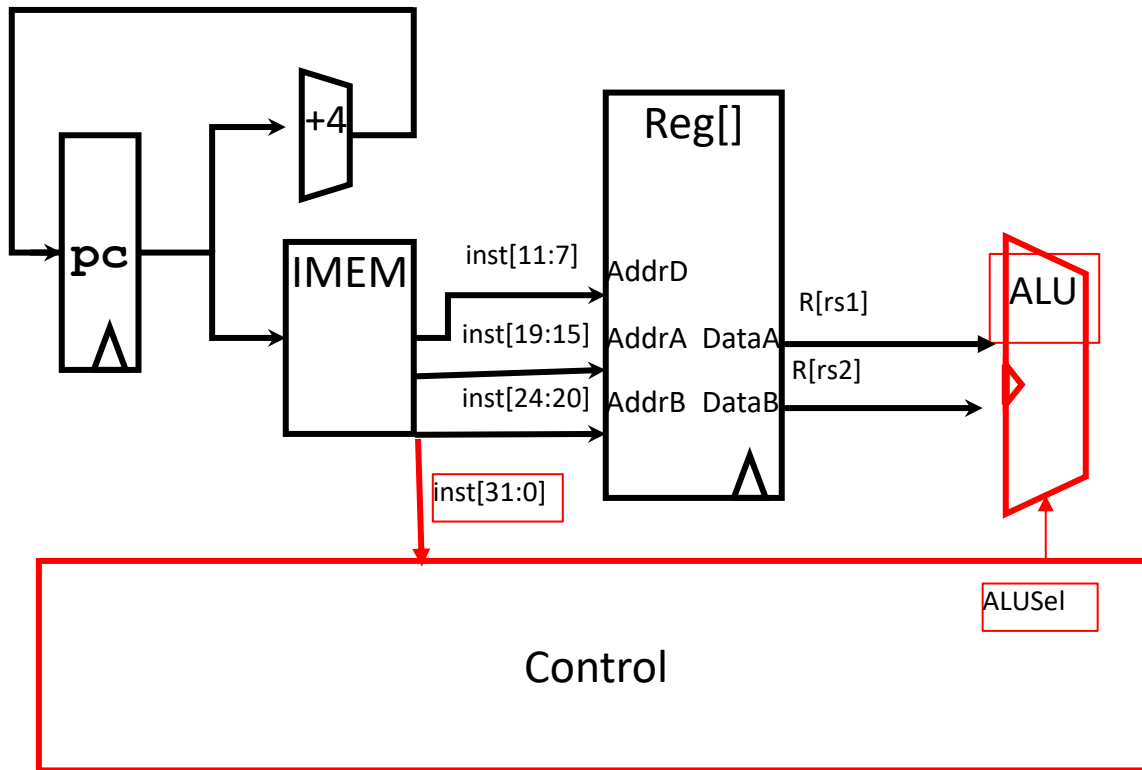


(4) Perform operation

- New hardware: ALU (Arithmetic Logic Unit)
- Abstraction for adders, multipliers, dividers, etc.
- How do we know what operation to execute?
 - Our first control bit! $ALUSel(ect)$

Adding addi to datapath

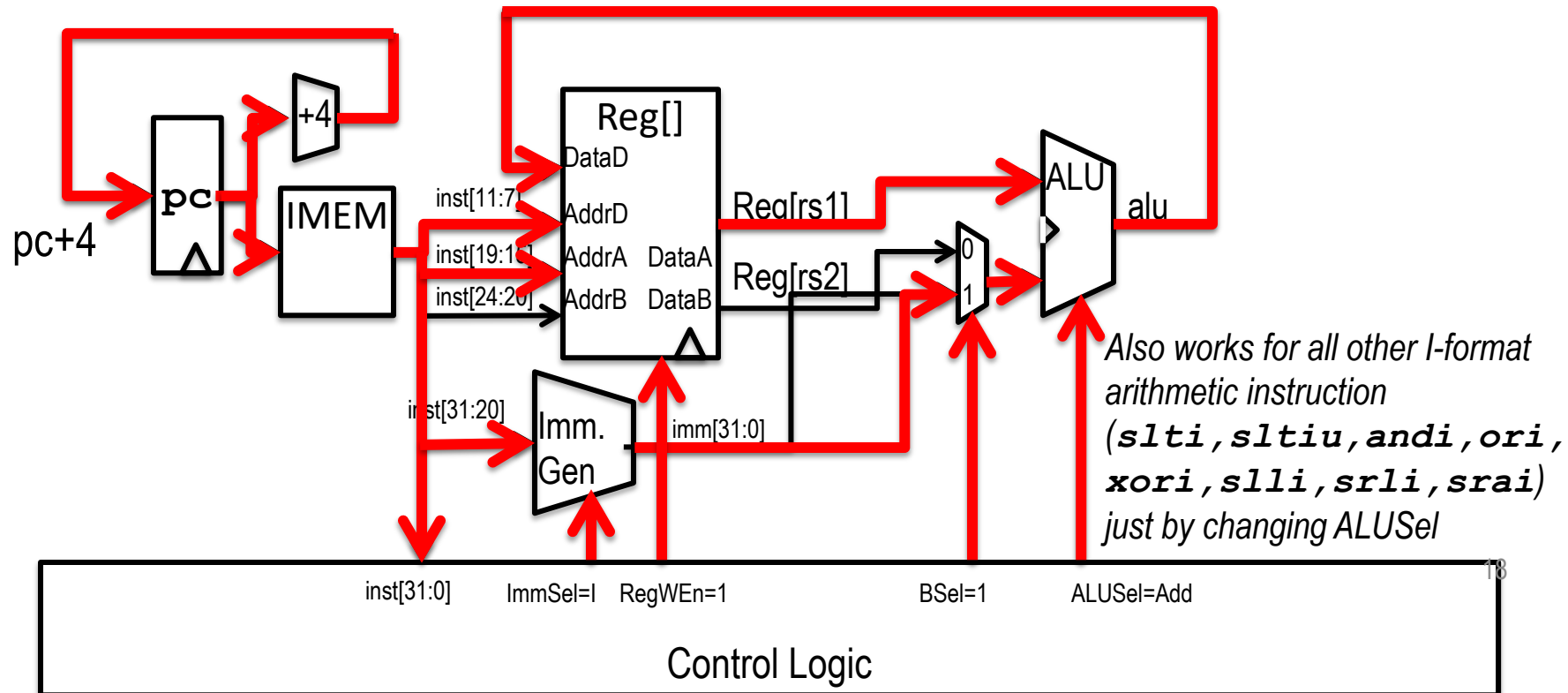


Adding lw to datapath

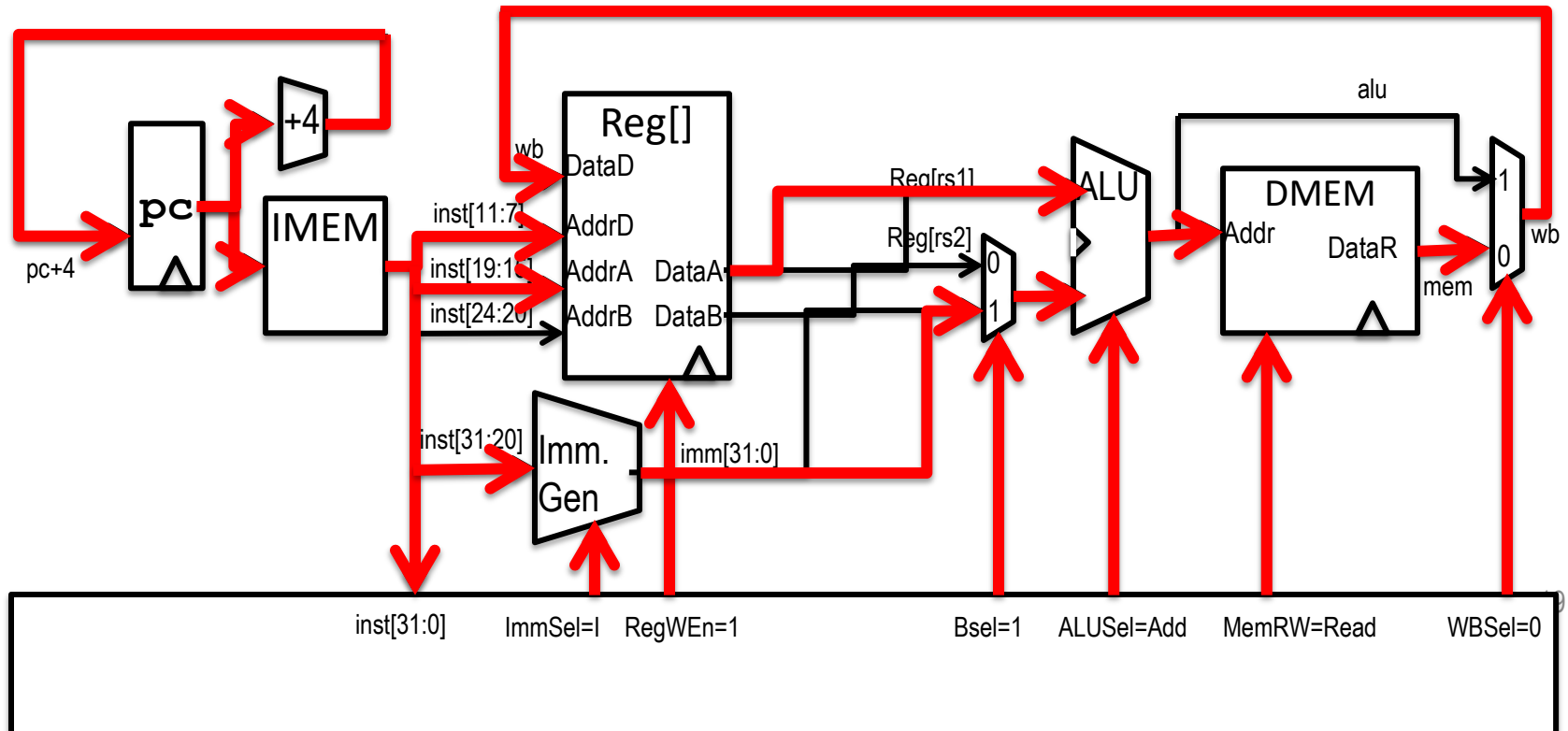


Storage Element: Idealized Memory


- Memory (idealized)
 - One input port: Data In
 - One output port: **Data Out**
- Memory access:
 - Read: Write Enable = 0, data at Address is placed on **Data Out**
 - Write: Write Enable = 1, Data In written to Address
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read, behaves as a combinational logic block: Address valid → **Data Out** valid after “access time”

 


Current Datapath

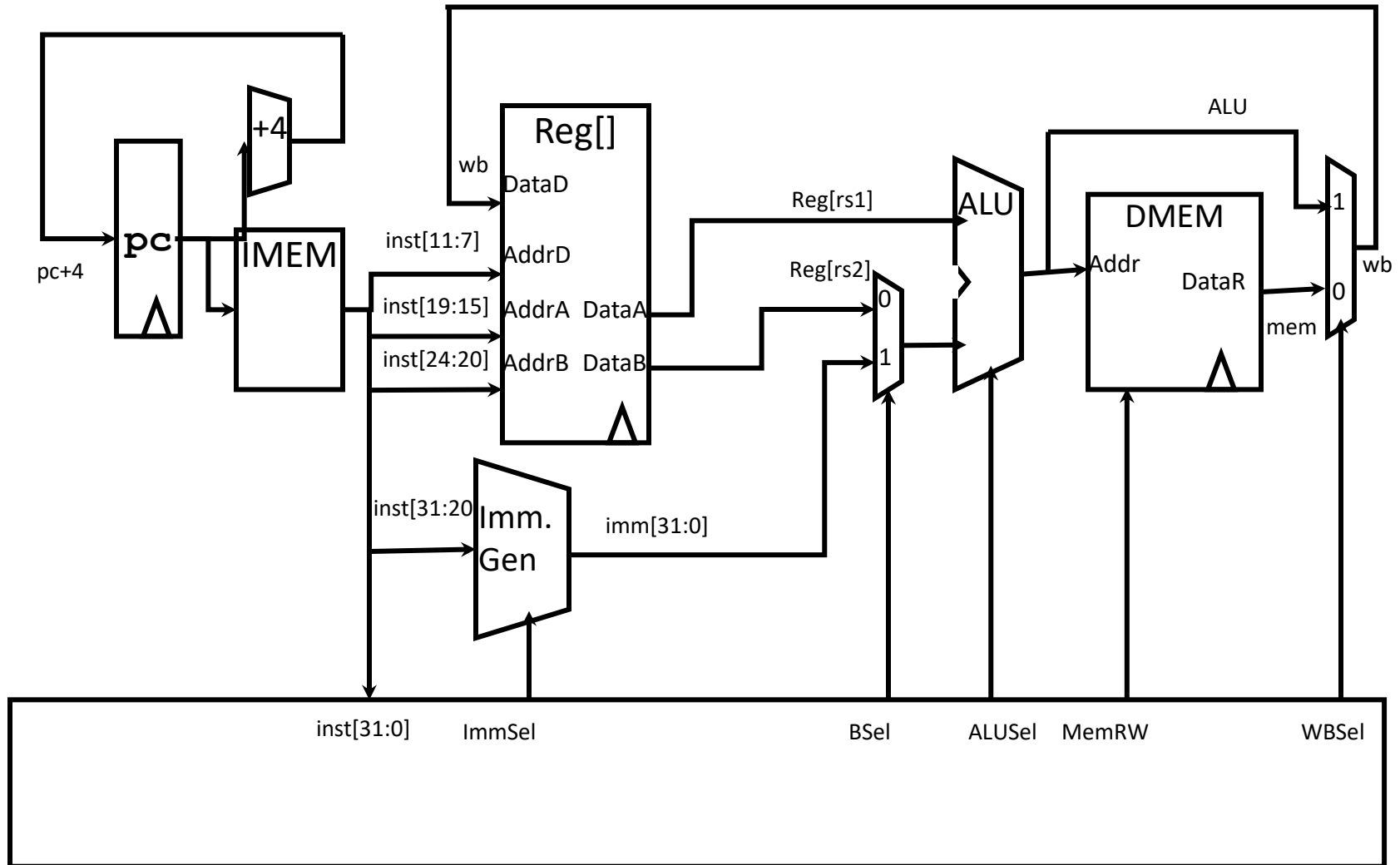


Adding sw to datapath

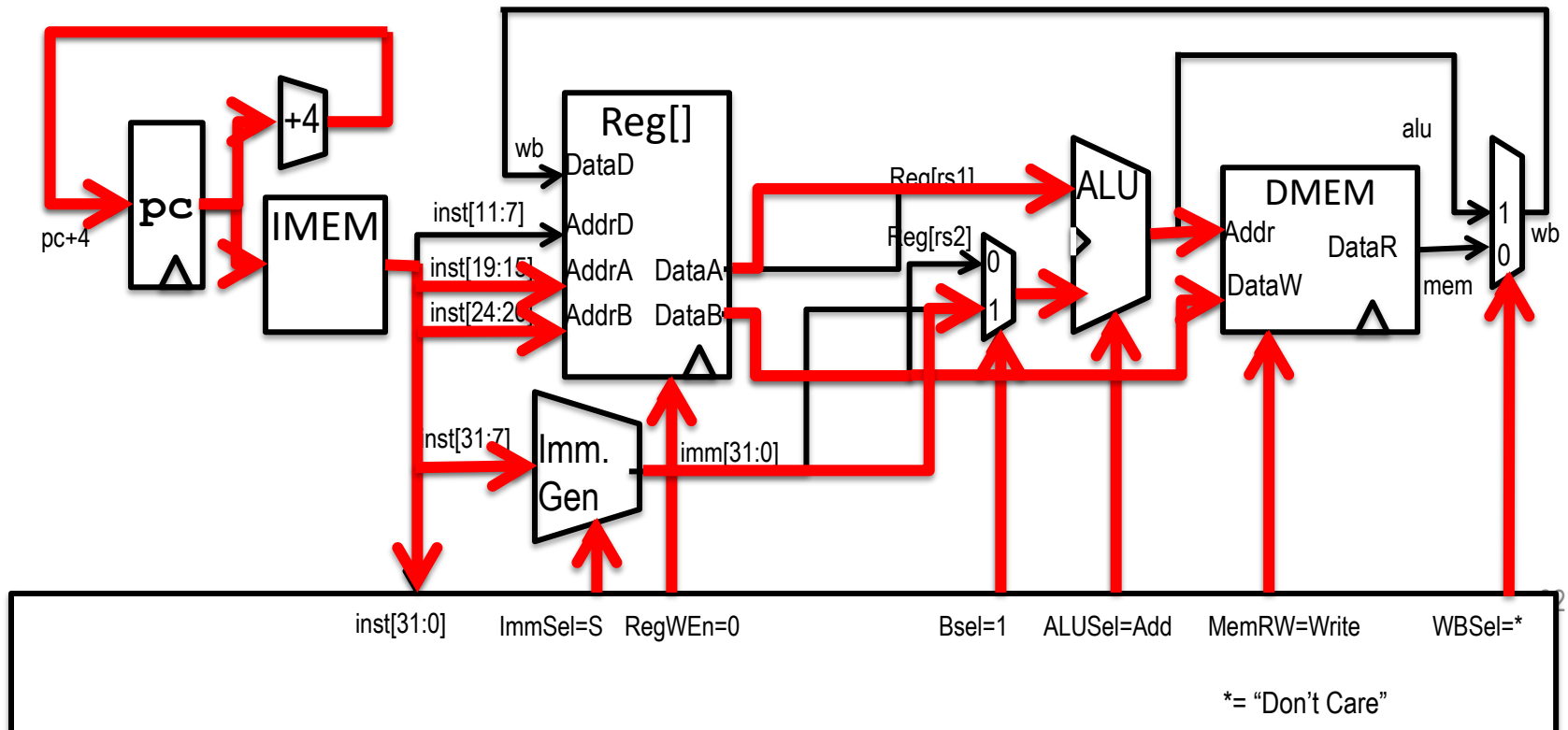


Adding branches to datapath

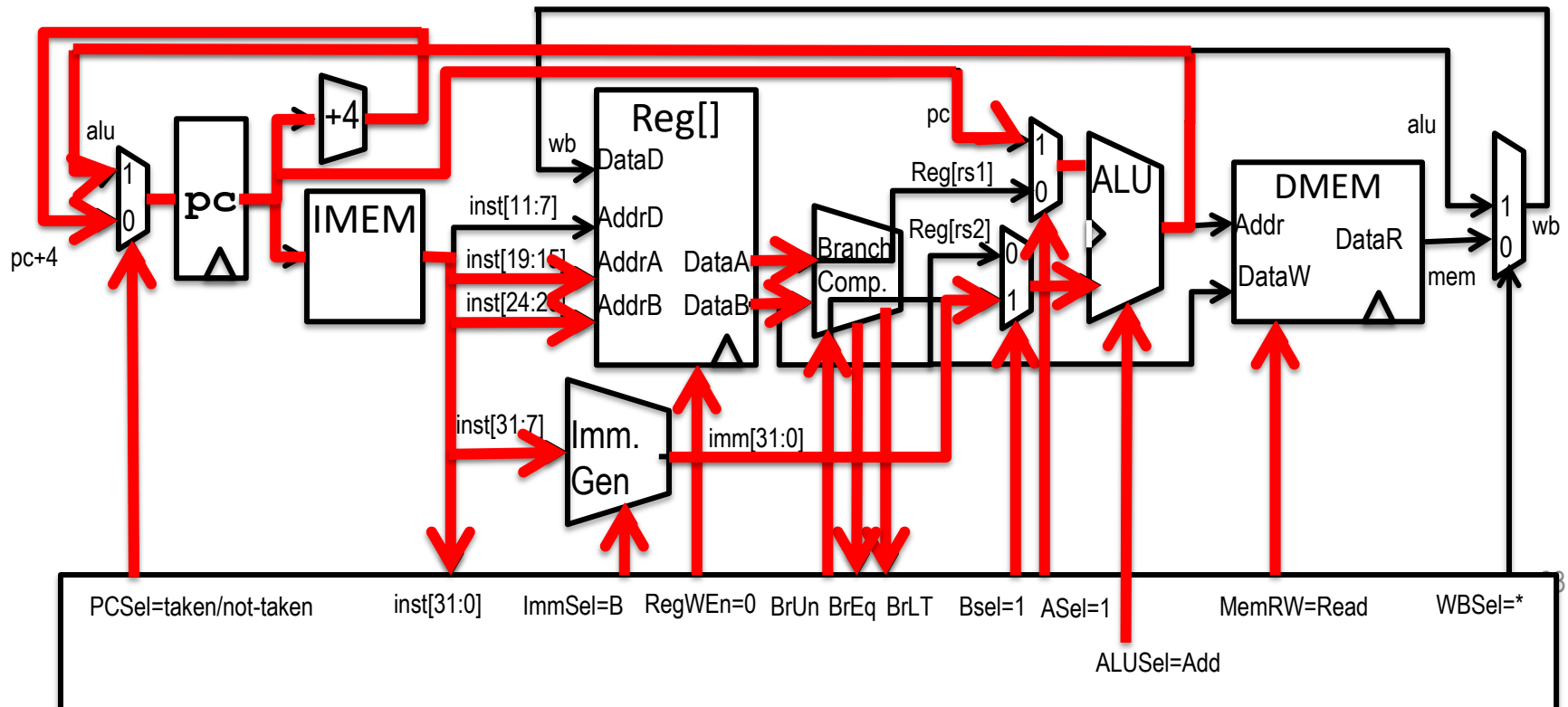


Adding jalr to datapath

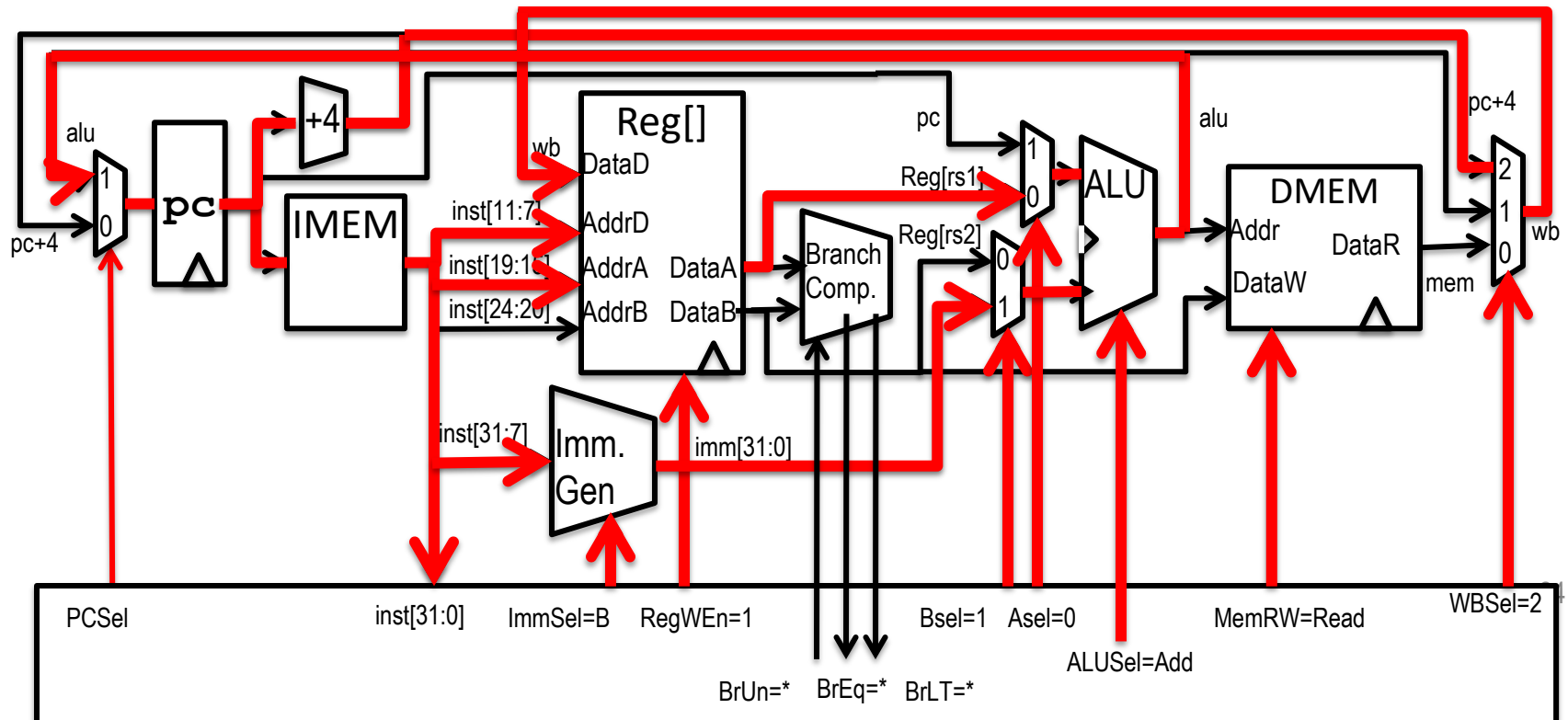

Adding jal to datapath

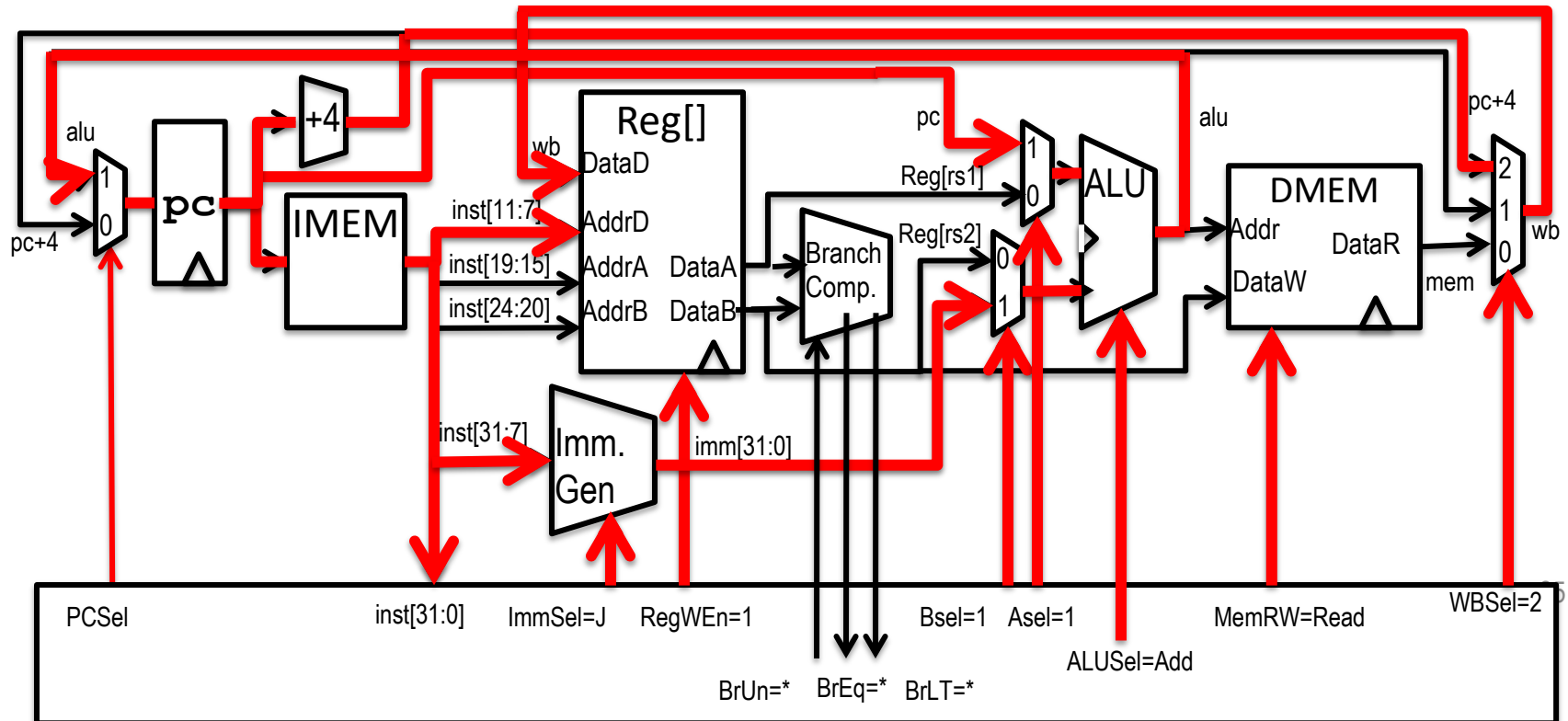

Implementing lui

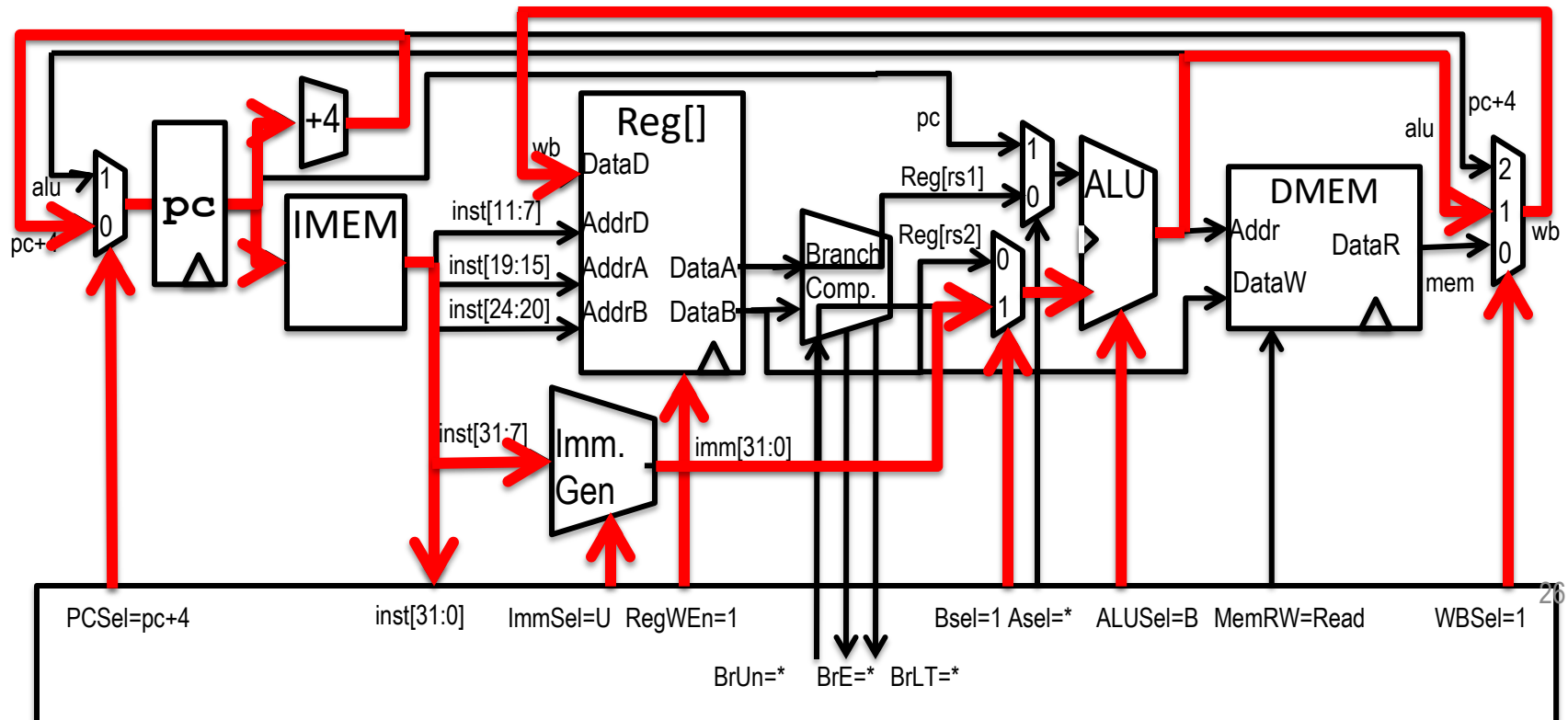

Implementing `auipc`

