

On the CNOT-complexity of CNOT-PHASE circuits

Matthew Amy ^{1,2} Parsiad Azimzadeh ² Michele Mosca ^{1,2}

¹Institute for Quantum Computing, Waterloo, Canada

²University of Waterloo, Waterloo, Canada

Theory of Quantum Computation,
Communication and Cryptography
July 18th, 2018

CNOT



Sea knot???

CNOT/CZ optimization problems

| Gate set | Complexity | State-of-the-art |
|---------------|------------|---|
| CNOT | ??? | Asymptotically optimal synthesis ¹ |
| CZ-PHASE | Polynomial | Optimal synthesis |
| CNOT-PHASE | ??? | Re-write rules |
| Clifford | ??? | Re-write rules |
| Clifford+ T | ??? | Re-write rules |


Assuming completely connected topology...

CNOT-PHASE: Circuits over CNOT and $R_Z(\theta) = \begin{pmatrix} 1 & 0 \\ 0 & e^{2\pi i \theta} \end{pmatrix}$

¹Patel, Markov and Hayes, *Optimal synthesis of linear reversible circuits*


Why CNOT-PHASE?

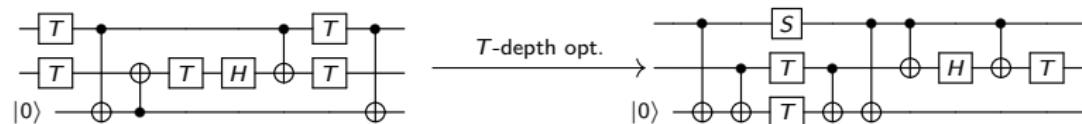Phase folding/ T -par uses T -depth optimal CNOT-PHASE synthesis as a sub-routine



Why CNOT-PHASE?

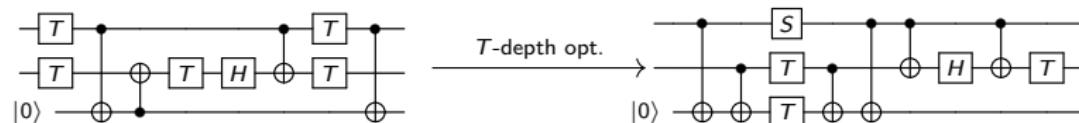Phase folding/ T -par uses T -depth optimal CNOT-PHASE synthesis as a sub-routine



Idea: replace T -depth optimal with CNOT-optimal!



Overview

We...

- ▶ Show that in certain cases, minimizing the number of CNOT gates is equivalent to finding a minimal CNOT circuit cycling through a set of parities of the inputs
- ▶ Show that cycling through a set of parities is NP-hard if
 - ▶ all CNOT gates have the same target, or
 - ▶ the circuit inputs are not linearly independent
- ▶ Give a new heuristic optimization algorithm

Introduction

Parity networks

Complexity of minimal parity network synthesis

Heuristic synthesis

Experiments

Conclusion

The sum-over-paths form

Recall the basis state action of CNOT and Phase gates:

$$\text{CNOT} : |x\rangle|y\rangle \mapsto |x\rangle|x \oplus y\rangle$$

$$R_Z(\theta) : |x\rangle \mapsto e^{2\pi i \theta x} |x\rangle$$

We call this basis state action the **sum-over-paths (SOP) form**

The sum-over-paths form

Recall the basis state action of CNOT and Phase gates:

$$\text{CNOT} : |x\rangle|y\rangle \mapsto |x\rangle|x \oplus y\rangle$$

$$R_Z(\theta) : |x\rangle \mapsto e^{2\pi i \theta x}|x\rangle$$

We call this basis state action the **sum-over-paths (SOP) form**

Definition

The SOP form of a CNOT-PHASE circuit C is a pair (f, A) where


- $f : \mathbb{F}_2^n \rightarrow \mathbb{R}$ is a pseudo-Boolean function given by

$$f(\mathbf{x}) = \sum_{\mathbf{y} \in \mathbb{F}_2^n} \hat{f}(\mathbf{y}) \chi_{\mathbf{y}}(\mathbf{x}), \quad \chi_{\mathbf{y}}(\mathbf{x}) = x_1 y_1 \oplus \cdots \oplus x_n y_n$$

- $A \in \text{GL}(n, \mathbb{F}_2)$ is a linear permutation such that $U_C : |\mathbf{x}\rangle \mapsto e^{2\pi i f(\mathbf{x})} |A\mathbf{x}\rangle$


Computing the sum-over-paths

Consider an implementation of CCZ:

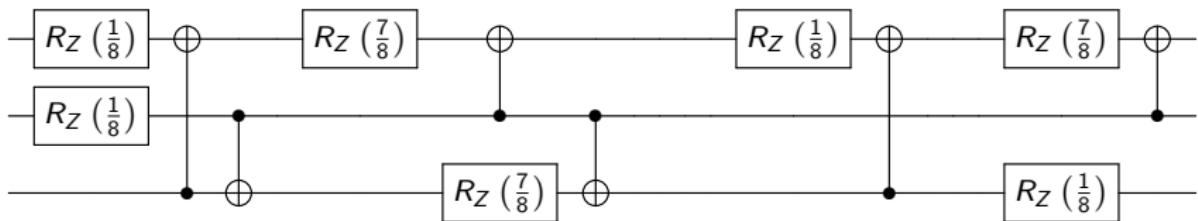


Computing the circuit sum-over-paths

First annotate...

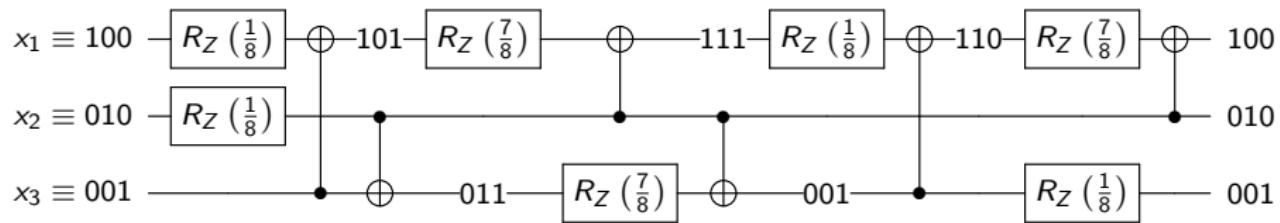

Computing the circuit sum-over-paths

First annotate...

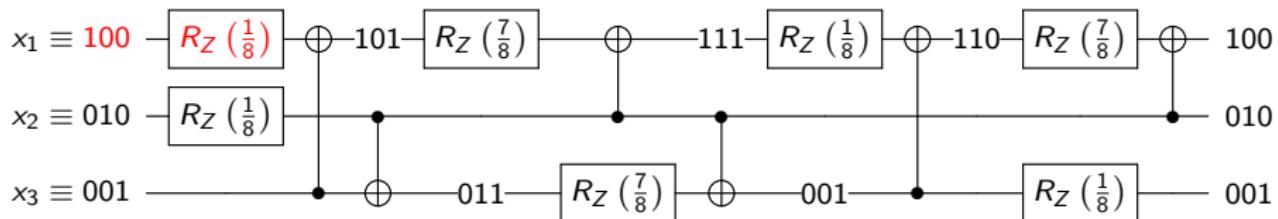


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1 + \dots)} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

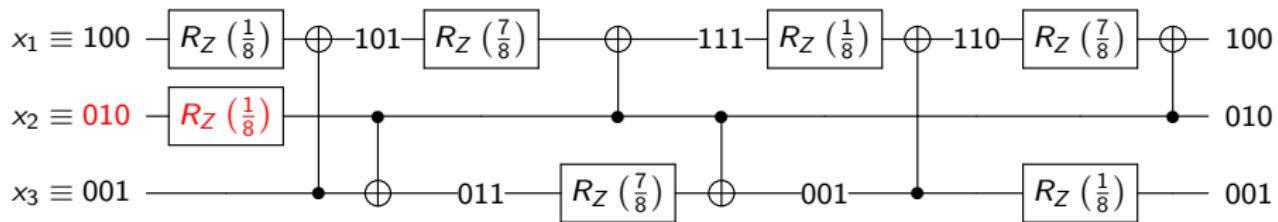


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2)} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

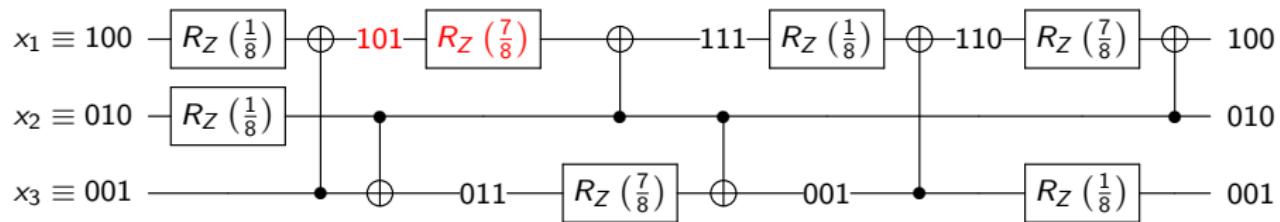


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3))} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

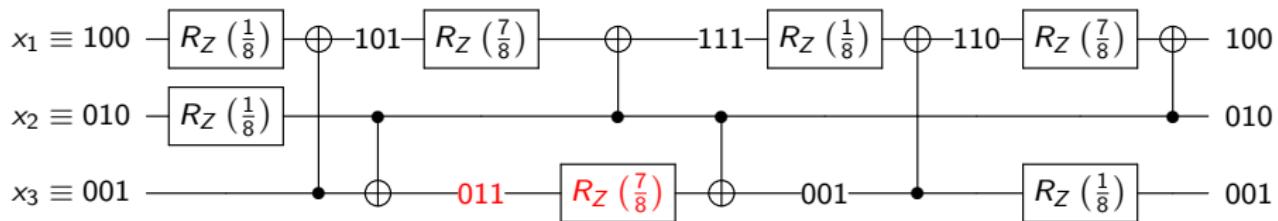


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3)+7(x_2 \oplus x_3))} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

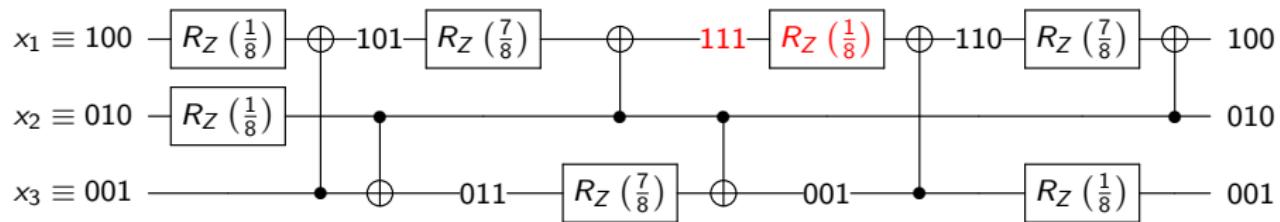


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3)+7(x_2 \oplus x_3)+(x_1 \oplus x_2 \oplus x_3))} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

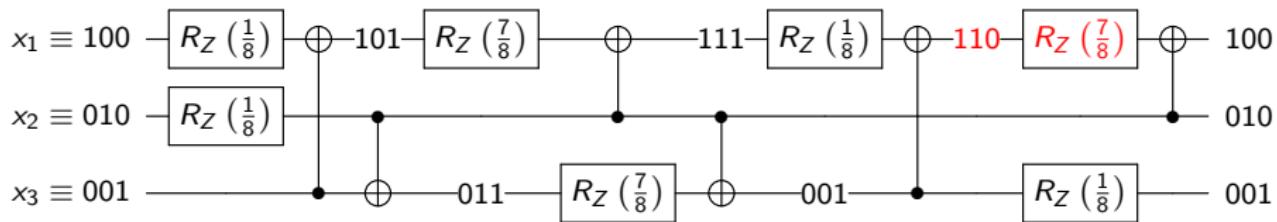


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3)+7(x_2 \oplus x_3)+(x_1 \oplus x_2 \oplus x_3)+7(x_1 \oplus x_2))} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

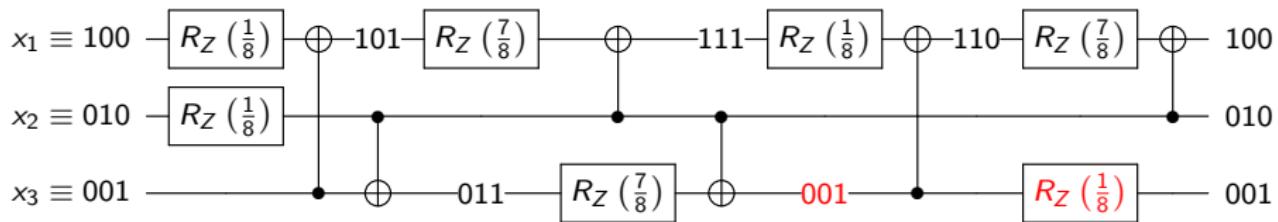


...Then add the phase factors

$$|x\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3)+7(x_2 \oplus x_3)+(x_1 \oplus x_2 \oplus x_3)+7(x_1 \oplus x_2)+x_3)} |x\rangle$$

Computing the circuit sum-over-paths

First annotate...

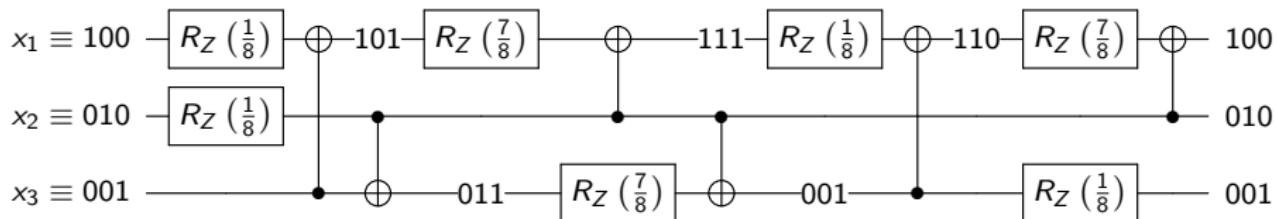

...Then add the phase factors

$$|\mathbf{x}\rangle \mapsto e^{\frac{2\pi i}{8}(x_1+x_2+7(x_1 \oplus x_3)+7(x_2 \oplus x_3)+(x_1 \oplus x_2 \oplus x_3)+7(x_1 \oplus x_2)+x_3)} |\mathbf{x}\rangle$$


$$\mapsto e^{\frac{2\pi i}{2}x_1x_2x_3} |\mathbf{x}\rangle$$

An observation

Recall:

$$\begin{aligned}CS^\dagger : |x_1 x_2\rangle &\mapsto e^{\frac{2\pi i}{4} 3x_1 x_2} |x_1 x_2\rangle \\&\mapsto e^{\frac{2\pi i}{8} (7x_1 + 7x_2 + x_1 \oplus x_2)} |x_1 x_2\rangle\end{aligned}$$

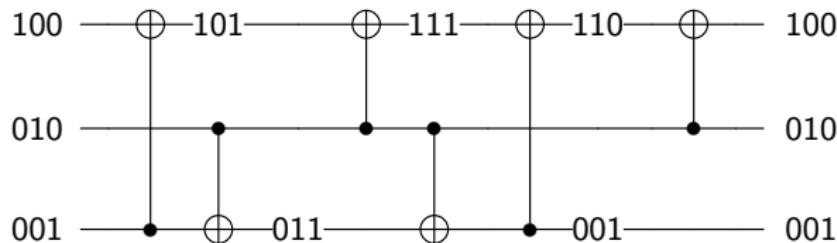Can use the same CNOT structure as CCZ to implement CS^\dagger !




An observation

Recall:

$$\begin{aligned}CS^\dagger : |x_1 x_2\rangle &\mapsto e^{\frac{2\pi i}{4} 3x_1 x_2} |x_1 x_2\rangle \\&\mapsto e^{\frac{2\pi i}{8} (\color{red}{7x_1} + \color{blue}{7x_2} + \color{green}{x_1 \oplus x_2})} |x_1 x_2\rangle\end{aligned}$$

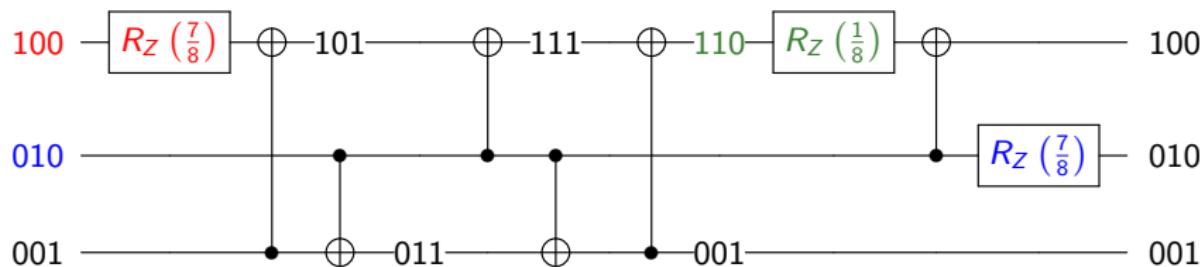Can use the same CNOT structure as CCZ to implement CS^\dagger !



Parity networks

Definition

A **parity network** for a set $S \subseteq \mathbb{F}_2^n$ is an n -qubit circuit C over CNOT gates where each $y \in S$ appears in the annotated circuit.

A parity network is **pointed at** $A \in \mathrm{GL}(n, \mathbb{F}_2)$ if it implements the overall linear transformation A .


Parity networks

Definition

A **parity network** for a set $S \subseteq \mathbb{F}_2^n$ is an n -qubit circuit C over CNOT gates where each $y \in S$ appears in the annotated circuit.

A parity network is **pointed at** $A \in \mathrm{GL}(n, \mathbb{F}_2)$ if it implements the overall linear transformation A .

E.g. the CNOT gates of CCZ ,

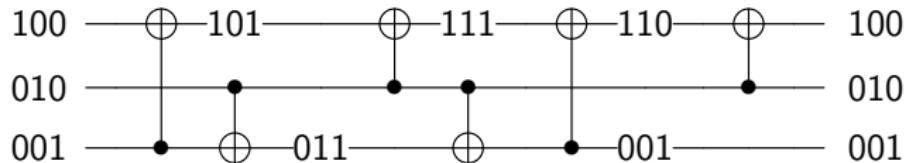

is a parity network for $S = \{100, 010, 001, 110, 101, 011, 111\}$
pointed at $A = I$

CNOT-minimal synthesis and parity networks

A CNOT-minimal circuit with SOP form (f, A) **necessarily** gives a minimal parity network for $\text{supp}(\hat{f})$ pointed at A

CNOT-minimal synthesis and parity networks

However...


CNOT-minimal synthesis and parity networks

A minimal parity network for $\text{supp}(\hat{f})$ may not give a CNOT-minimal circuit **across equivalent SOP forms**

CNOT-minimal synthesis and parity networks

A minimal parity network for $\text{supp}(\hat{f})$ may not give a CNOT-minimal circuit **across equivalent SOP forms**

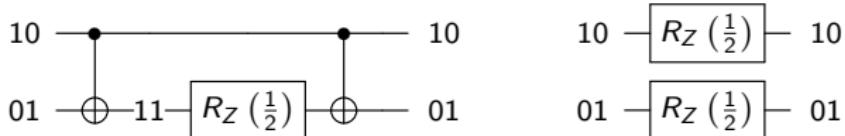E.g., $(\frac{1}{2}(x_1 \oplus x_2), I)$ and $(\frac{1}{2}x_1 + \frac{1}{2}x_2, I)$ give equivalent unitaries but have minimal parity network implementations



Main result

Theorem

CNOT minimization of CNOT-PHASE circuits is at least as hard as synthesizing a minimal parity network

Main result

Theorem

CNOT minimization of CNOT-PHASE circuits is at least as hard as synthesizing a minimal parity network

Intuition:

- If $(f, A) \sim (f', A')$, then $A = A'$ and $f' = f + k$ for $k : \mathbb{F}_2^n \rightarrow \mathbb{Z}$

Main result

Theorem

CNOT minimization of CNOT-PHASE circuits is at least as hard as synthesizing a minimal parity network

Intuition:

- ▶ If $(f, A) \sim (f', A')$, then $A = A'$ and $f' = f + k$ for $k : \mathbb{F}_2^n \rightarrow \mathbb{Z}$
- ▶ The Fourier coefficients of k have even order in \mathbb{R}/\mathbb{Z}

Main result

Theorem

CNOT minimization of CNOT-PHASE circuits is at least as hard as synthesizing a minimal parity network

Intuition:

- ▶ If $(f, A) \sim (f', A')$, then $A = A'$ and $f' = f + k$ for $k : \mathbb{F}_2^n \rightarrow \mathbb{Z}$
- ▶ The Fourier coefficients of k have even order in \mathbb{R}/\mathbb{Z}
- ▶ If no elements of \widehat{f} have even order in \mathbb{R}/\mathbb{Z} , then

$$\text{supp}(\widehat{f}') \subseteq \text{supp}(\widehat{f})$$

Introduction

Parity networks

Complexity of minimal parity network synthesis

Heuristic synthesis

Experiments

Conclusion

Minimal parity network synthesis is hard...?

Goal:

*Prove that the minimal parity network problem (MPNP)
is NP-hard*


Obvious reductions don't work due to **shortcuts**

Minimal parity network synthesis is hard...?


Goal:

Prove that the minimal parity network problem (MPNP) is NP-hard

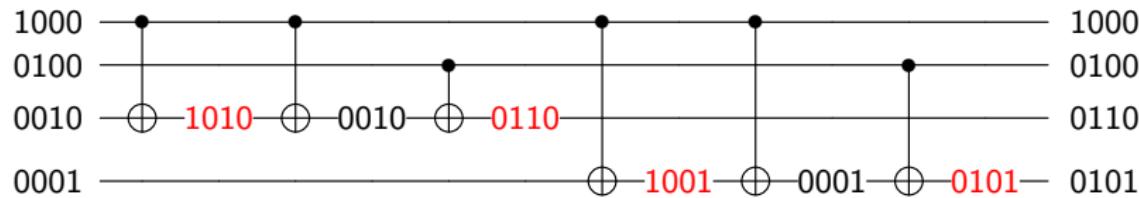
Obvious reductions don't work due to **shortcuts**



vs.

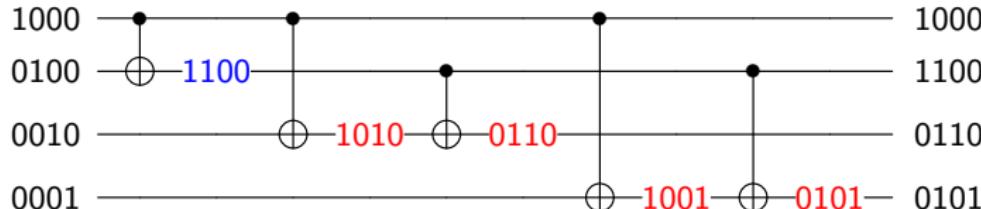

A graphical interpretation

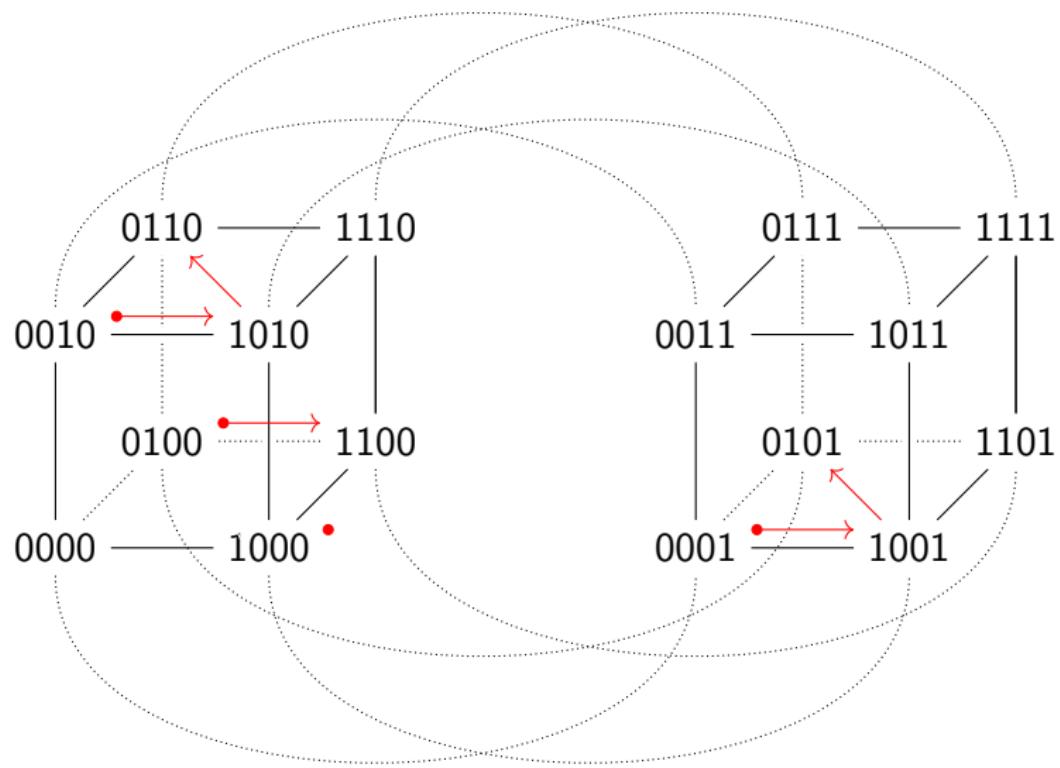

Fixed-target minimal parity network


Conjecture

If for all $\mathbf{y} \in S$, $y_i = 1$, then there exists a minimal parity network for S where each CNOT targets bit i .


Fixed-target minimal parity network

Conjecture

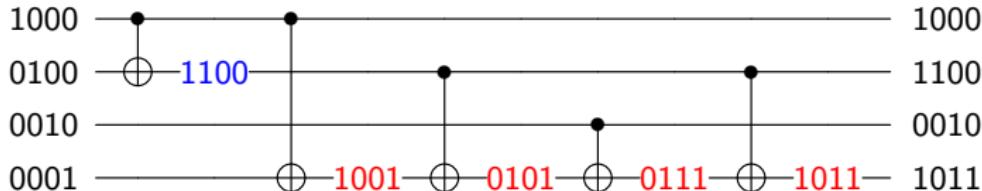If for all $y \in S$, $y_i = 1$, then there exists a minimal parity network for S where each CNOT targets bit i .



vs.

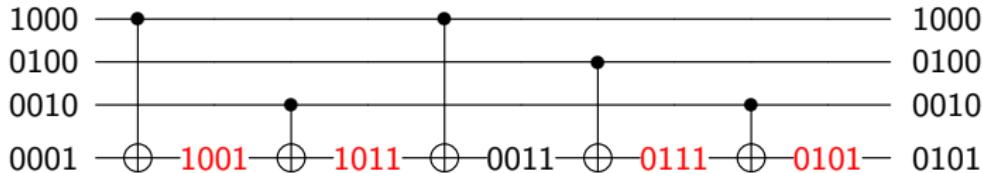

Fixed-target minimal parity network

Theorem

The fixed-target minimal parity network problem is NP-complete

Proof:


Reduction from traveling salesman on the hypercube ²

²Ernvall, Katajainen, and Penttonen, *NP-completeness of the Hamming salesman problem*


Minimal parity network with encoded inputs

If some inputs are linearly dependent, fewer gates may be needed to implement a parity network

E.g., $S = \{111\}$

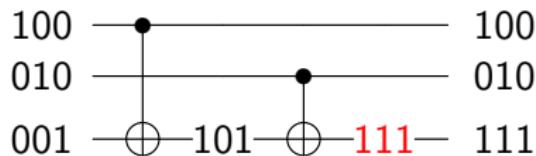


vs.

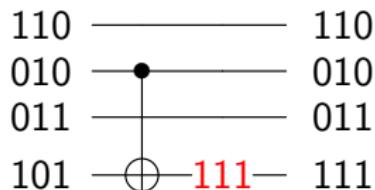


Minimal parity network with encoded inputs

If some inputs are linearly dependent, fewer gates may be needed to implement a parity network

E.g., $S = \{111\}$

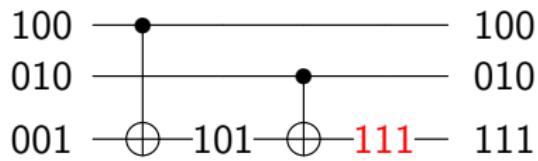

vs.

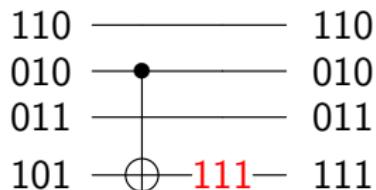

Direct applications to phase folding with ancillas!

Minimal parity network with encoded inputs

Theorem

The encoded input minimal parity network problem is NP-complete

Proof:

Reduction from maximum-likelihood decoding³

³Berlekamp, McEliece, and van Tilborg, *On the inherent intractability of certain coding problems*

Introduction

Parity networks

Complexity of minimal parity network synthesis

Heuristic synthesis

Experiments

Conclusion

Problem statement


Given $S \subseteq \mathbb{F}_2^n$, synthesize an efficient parity network for S

Bases cases

For $S = \mathbb{F}_2^n \parallel x$, $x \in \mathbb{F}_2^m$, minimal parity network is the Gray code and can be computed greedily

E.g.,
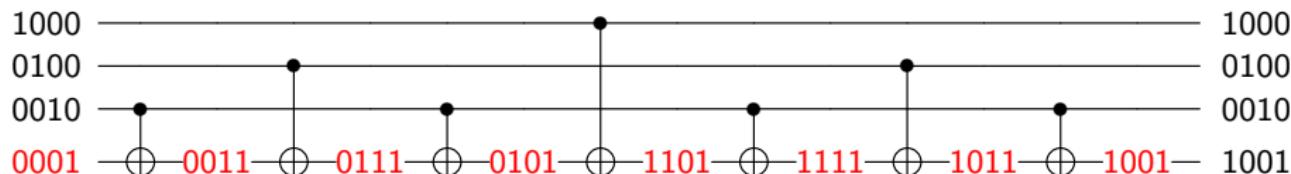
$$S = \mathbb{F}_2^3 \parallel 1 = \{0001, 1001, 0101, 1101, 0011, 1011, 0111, 1111\}$$




Bases cases


For $S = \mathbb{F}_2^n$, case is similar

E.g.,

$$S = \mathbb{F}_2^3$$

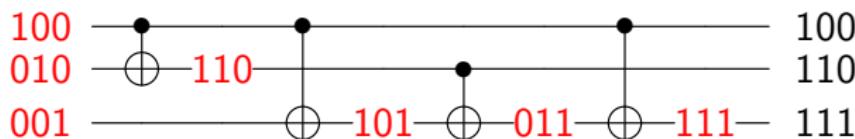

$$S = \mathbb{F}_2^4$$

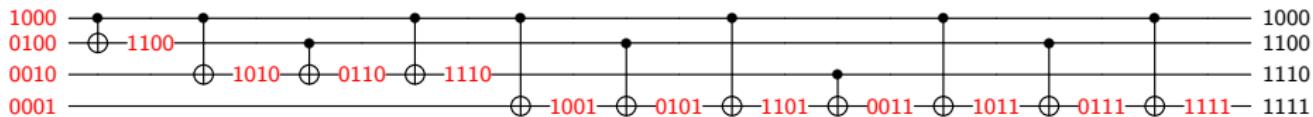

The GRAY-SYNTH algorithm

Main idea:

Try to identify subsets S' of S which have the form $S' \simeq \mathbb{F}_2^n \parallel x$, and synthesize those greedily

The GRAY-SYNTH algorithm

1. Start with a singleton stack containing the set S
2. Pop a set S' off the stack
3. If $x_i \oplus x_j$ appears in every parity of S' ,
 - ▶ Apply a CNOT between bits i and j , and
 - ▶ Adjust all subsets remaining on the stack accordingly
4. Pick some row i maximizing the number of parities in S' which **either contain or do not contain** x_i
5. Set $S_b = \{x \in S' \mid x_i = b\}$ and push S_1, S_0 onto the stack
6. Go to step 2

Invariant: remaining parities are expressed over the current basis

- ▶ Avoids “uncomputing” or backtracking

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{cccccc} 0 & 1 & 1 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 1 & 0 \end{array} \right\}$$

$$\left\{ \begin{array}{ccccc} 1 & 1 & 1 & 1 & 1 \\ 0 & 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 \end{array} \right\}$$

$$\left\{ \begin{array}{cccc} 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 \end{array} \right\}$$

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{c|cccccc} 0 & 1 & 1 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 1 & 0 \end{array} \right\}$$

- ▶ Columns are remaining parities
- ▶ Box is current top of the stack
- ▶ White rows haven't been partitioned
- ▶ Grey rows have been partitioned

Example


Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{c|cccccc} 0 & 1 & 1 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 1 & 0 \end{array} \right\}$$

- ▶ Columns are remaining parities
- ▶ Box is current top of the stack
- ▶ White rows haven't been partitioned
- ▶ Grey rows have been partitioned

Example


Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$
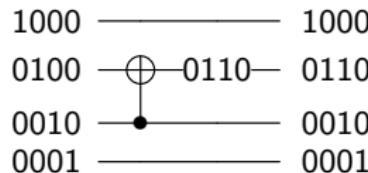
$$\left\{ \begin{array}{|c|cccccc|} \hline 0 & 1 & 1 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 & 0 & 0 \\ \hline 0 & 0 & 1 & 0 & 1 & 0 \\ \hline \end{array} \right\} \rightarrow \left\{ \begin{array}{|c|cccccc|} \hline 0 & 1 & 1 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 & 1 & 1 \\ \hline \textcolor{red}{0} & 0 & 0 & \textcolor{red}{0} & \textcolor{red}{1} & \textcolor{red}{1} \\ \hline 0 & 0 & 1 & 0 & 1 & 0 \\ \hline \end{array} \right\}$$


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

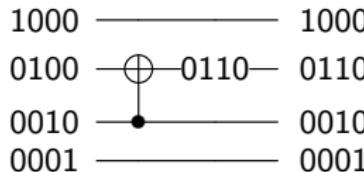
$$\left\{ \begin{array}{c|cccccc} & 1 & 1 & 1 & 1 & 1 \\ \hline 0 & 1 & 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 1 & 0 \end{array} \right\}$$


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|cc|ccc|} \hline & & 1 & 1 & 1 \\ \hline 1 & 1 & 0 & 0 & 1 & 1 & 1 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 \\ \hline \end{array} \right\}$$

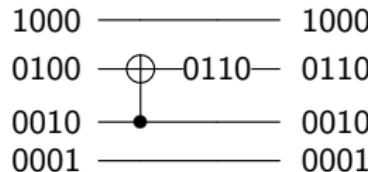


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|c|} \hline 1 & 1 \\ \hline 0 & 0 \\ \hline 0 & 0 \\ \hline 0 & 1 \\ \hline \end{array} \middle| \begin{array}{ccc} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 0 & 1 & 1 \\ 0 & 1 & 0 \\ \hline \end{array} \right\}$$

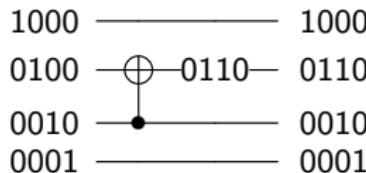


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|ccccc|} \hline & 1 & 1 & 1 & 1 & 1 \\ \hline 0 & 0 & 1 & 1 & 1 \\ 0 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 1 & 0 \\ \hline \end{array} \right\}$$

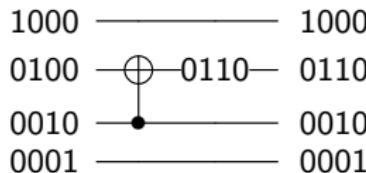


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|cccc} \hline & 1 & 1 & 1 \\ \hline 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 \\ \hline \end{array} \right\} \rightarrow \left\{ \begin{array}{|c|cccc} \hline & 1 & 1 & 1 & 1 \\ \hline 0 & 1 & 1 & 1 & 1 \\ 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 & 1 \\ \hline \end{array} \right\}$$

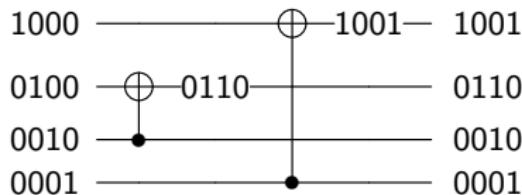


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|ccc|} \hline 1 & 1 & 1 \\ 1 & 1 & 1 \\ \hline 0 & 1 & 1 \\ 1 & 0 & 1 \\ \hline \end{array} \right\} \rightarrow \left\{ \begin{array}{|ccc|} \hline 1 & 1 & 1 \\ \textcolor{red}{0} & \textcolor{red}{0} & \textcolor{red}{0} \\ \hline 0 & 1 & 1 \\ 1 & 0 & 1 \\ \hline \end{array} \right\}$$

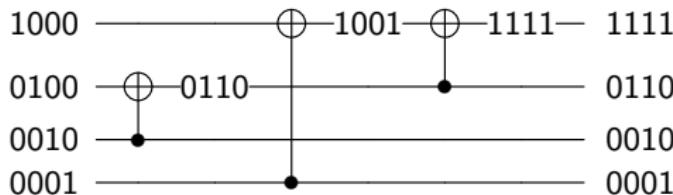


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|ccc|} \hline & 1 & 1 & \\ \hline 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & \\ \hline 1 & 0 & 1 & \\ \hline \end{array} \right\}$$

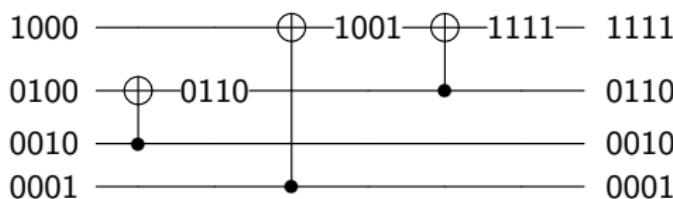


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|ccc|} \hline & 1 & 1 & 1 \\ \hline 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 1 \\ \hline 1 & 0 & 1 & 0 \\ \hline \end{array} \right\} \rightarrow \left\{ \begin{array}{|c|ccc|} \hline & 1 & 1 & 1 \\ \hline 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 1 \\ \hline \textcolor{red}{0} & \textcolor{red}{1} & \textcolor{red}{0} & \textcolor{red}{0} \\ \hline \end{array} \right\}$$

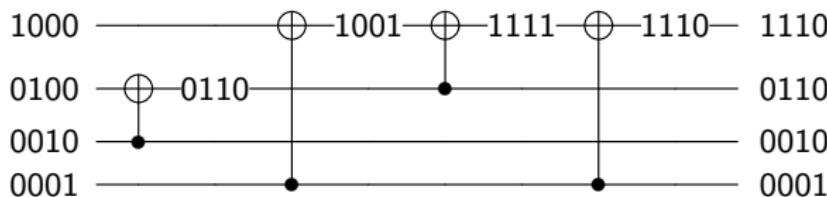


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|c|} \hline 1 & 1 \\ \hline 0 & 0 \\ \hline 1 & 1 \\ \hline 1 & 0 \\ \hline \end{array} \right\} \rightarrow \left\{ \begin{array}{|c|c|} \hline 1 & 1 \\ \hline 0 & 0 \\ \hline \textcolor{red}{0} & \textcolor{red}{0} \\ \hline 1 & 0 \\ \hline \end{array} \right\}$$

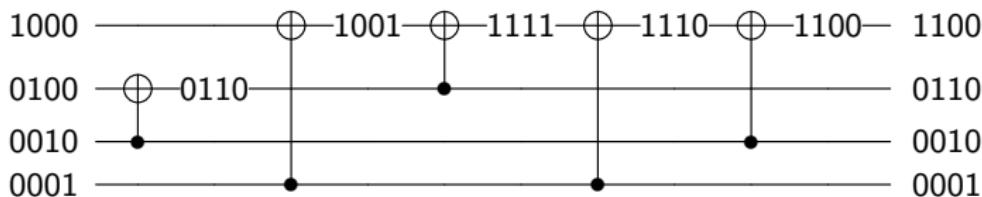


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{|c|c|} \hline 1 & 1 \\ \hline 0 & 0 \\ \hline 0 & 0 \\ \hline 1 & 0 \\ \hline \end{array} \right\}$$

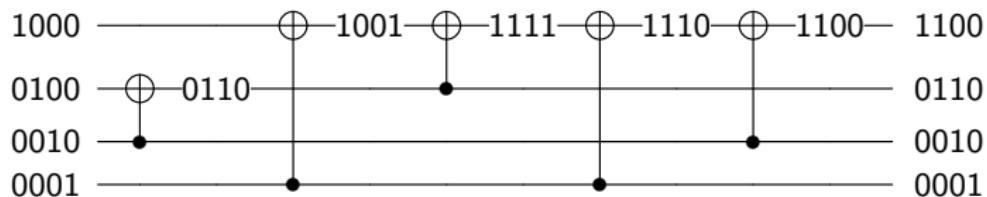


- ▶ Columns are remaining parities
- ▶ White rows haven't been partitioned
- ▶ Box is current top of the stack
- ▶ Grey rows have been partitioned

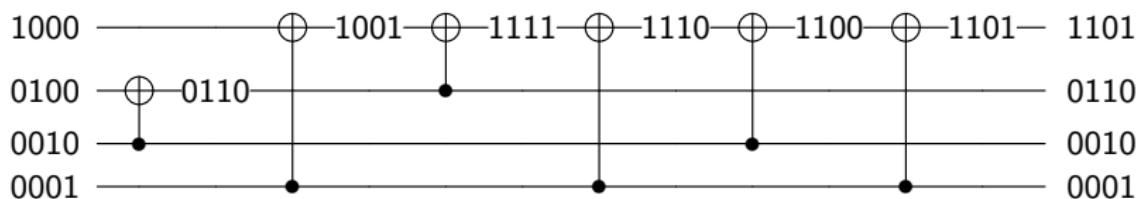Example

Parity network for $S = \{0110, 1000, 1001, 1110, 1101, 1100\}$

$$\left\{ \begin{array}{c} 1 \\ 0 \\ 0 \\ 1 \end{array} \right\} \rightarrow \left\{ \begin{array}{c} 1 \\ 0 \\ 0 \\ 0 \end{array} \right\}$$



- ▶ Columns are remaining parities
- ▶ Box is current top of the stack
- ▶ White rows haven't been partitioned
- ▶ Grey rows have been partitioned

Introduction

Parity networks


Complexity of minimal parity network synthesis

Heuristic synthesis

Experiments

Conclusion

Performance vs. brute force

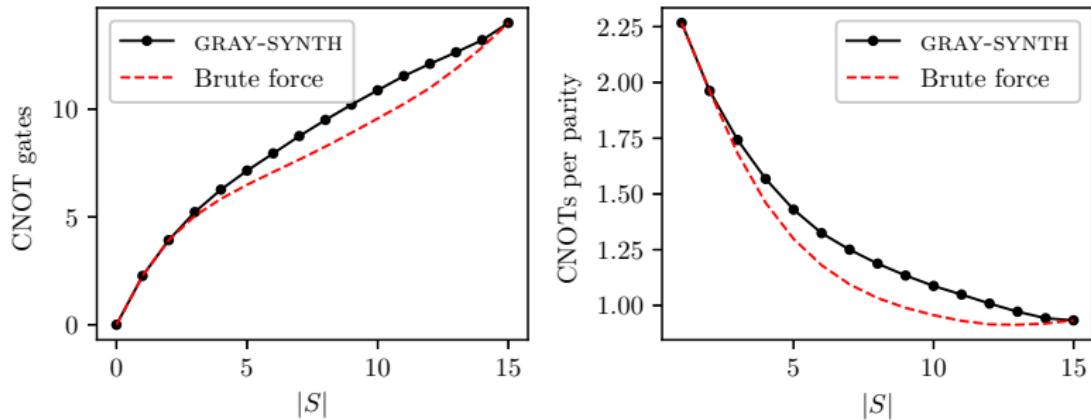

- ▶ Data collected across all sets of parities on 4 bits
- ▶ GRAY-SYNTH within 15% of optimal on average for $|S| = 8$

Benchmarks

| Benchmark | <i>n</i> | Base | Nam et al. (L) | | T-par (GRAY-SYNTH) | | |
|-----------------------------|----------|--------------|----------------|--------------|--------------------|--------------|-------|
| | | | CNOT | Time | CNOT | Time | CNOT |
| Grover_5 | 9 | 336 | — | — | 0.027 | 210 | 37.5 |
| Mod_5_4 | 5 | 32 | < 0.001 | 28 | 0.001 | 26 | 18.8 |
| VBE-Adder_3 | 10 | 80 | < 0.001 | 50 | 0.004 | 42 | 47.5 |
| CSLA-MUX_3 | 15 | 90 | < 0.001 | 76 | 0.073 | 100 | -11.1 |
| CSUM-MUX_9 | 30 | 196 | < 0.001 | 168 | 0.095 | 148 | 24.5 |
| QCLA-Com_7 | 24 | 215 | 0.001 | 132 | 0.097 | 136 | 36.7 |
| QCLA-Mod_7 | 26 | 441 | 0.004 | 302 | 0.145 | 356 | 19.3 |
| QCLA-Adder_10 | 36 | 267 | 0.002 | 195 | 0.112 | 189 | 29.2 |
| Adder_8 | 24 | 466 | 0.004 | 331 | 0.165 | 352 | 24.5 |
| RC-Adder_6 | 14 | 104 | < 0.001 | 73 | 0.080 | 71 | 31.7 |
| Mod-Red_21 | 11 | 122 | < 0.001 | 81 | 0.091 | 84 | 31.1 |
| Mod-Mult_55 | 9 | 55 | < 0.001 | 40 | 0.004 | 45 | 18.2 |
| Mod-Adder_1024 | 28 | 2005 | — | — | 0.739 | 1376 | 31.4 |
| Cycle_17_3 | 35 | 4532 | — | — | 2.618 | 2998 | 36.8 |
| GF(2^{32})-Mult | 96 | 7292 | 1.834 | 6299 | 5.571 | 6658 | 8.7 |
| GF(2^{64})-Mult | 192 | 28861 | 58.341 | 24765 | 114.310 | 25966 | 10.0 |
| Ham_15 (low) | 17 | 259 | — | — | 0.043 | 208 | 19.7 |
| Ham_15 (med) | 17 | 574 | — | — | 0.089 | 351 | 43.0 |
| Ham_15 (high) | 20 | 2489 | — | — | 0.376 | 1500 | 40.0 |
| HWB_6 | 7 | 131 | — | — | 0.006 | 111 | 15.3 |
| HWB_8 | 12 | 7508 | — | — | 1.706 | 6719 | 10.5 |
| QFT_4 | 5 | 48 | — | — | 0.005 | 47 | 2.1 |
| $\Lambda_5(X)$ | 9 | 49 | < 0.001 | 30 | 0.003 | 30 | 38.8 |
| $\Lambda_5(X)$ (Barenco) | 9 | 84 | < 0.001 | 60 | 0.004 | 54 | 35.7 |
| $\Lambda_{10}(X)$ | 19 | 119 | < 0.001 | 70 | 0.071 | 70 | 41.2 |
| $\Lambda_{10}(X)$ (Barenco) | 19 | 224 | 0.001 | 160 | 0.029 | 144 | 35.7 |
| Total | | | | | | | 23.3 |

Introduction

Parity networks

Complexity of minimal parity network synthesis

Heuristic synthesis

Experiments

Conclusion

Conclusion

In this talk...

- ▶ Parity networks characterize the CNOT complexity of CNOT-PHASE circuits **for a particular phase function**
- ▶ CNOT minimization is at least as hard as synthesizing a minimal parity network
- ▶ Synthesizing a minimal parity network is NP-hard when targets are fixed or inputs are encoded
- ▶ A heuristic parity network synthesis algorithm & benchmarks

Future work

- ▶ Proof of hardness for the general problem
- ▶ Synthesis algorithm that combines parity network synthesis with an output linear permutation
- ▶ Adding topology constraints

Thank you!