

Lecture 3

Circuit models of computation

Circuit models are simplistic (but powerful) models of computation based around **composition** of a (typically) finite set of basic operations called **gates**. **Wires** are used to compose gates by connecting inputs & outputs.

(Classical circuits)


In the classical circuit model,

- The state of a bit is 0 or 1
- The state of n bits is a **bitstring**
 $\vec{x} \in \{0,1\}^n$

- Computations are functions

$$f : \{0,1\}^n \longrightarrow \{0,1\}^m$$

 We describe functions graphically via **circuit diagrams**



A **gate** computes a fixed function with a fixed number of inputs and outputs

Ex.

The **NOT** gate computes the 1-bit function

$$f(a) = \neg a = 1 \oplus a$$


↑ addition mod 2: $0 \oplus 0 = 0$

$$0 \oplus 1 = 1$$

$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$

We draw the NOT gate as

 

Other gates are


 (**AND** gate, $f(a,b) = ab$)

 (**XOR** gate, $f(a,b) = a \oplus b$)

(Note: AND and XOR are multiplication and addition resp. in the Boolean field $\mathbb{Z}_2$ or $\mathbb{F}_2$)


Circuits are created by connecting the input and output wires

Ex.

 

↙ distributivity of mult.

 In the classical circuit model, we typically assume we can **copy** a bit, called **FANOUT**




Universality

A finite set G of gates is **universal** if any **Boolean function** $f: \{0,1\}^n \rightarrow \{0,1\}$ can be written as a circuit using only gates taken from G

Ex.

$$\text{Let } f(a,b,c) = a(1 \oplus b)c \oplus bc$$

 A circuit for f over $\{\text{AND}, \text{NOT}, \text{XOR}, \text{FANOUT}\}$ is



Thm.

$\{\text{AND}, \text{XOR}, \text{NOT}, \text{FANOUT}\}$ is universal

Proof

By induction on the number of inputs n

For $n=1$, there are 2 unique functions:


$$a \mapsto a$$

$$a \mapsto 1 \oplus a$$

For $n+1$ inputs, $n \geq 1$, we have the following equality

$$f(x_1, \dots, x_n, x_{n+1}) = (1 \oplus x_{n+1})f_0(x_1, \dots, x_n) \oplus x_{n+1}f_1(x_1, \dots, x_n)$$

We can thus implement f as follows

 

By the hypothesis, f_0 & f_1 can each be written over the gate set, so we're done $\square$


Note:

f_0 & f_1 are called **cofactors** of f , and the expression for f via its cofactors is called the **Shannon expansion** of f

(Translating between gate sets)

We can **translate** circuits written in one gate set to another gate set by replacing gates with equivalent circuits



Ex.

 

Given two gate sets G_1 & G_2 , if G_1 is universal and every gate of G_1 can be written as a circuit over G_2 , then G_2 is also universal

Ex.

  $\{\text{AND}, \text{XOR}, \text{FANOUT}\}$ is universal by the above
 $\{\text{NAND}, \text{FANOUT}\}$ is universal since



Aside: interpretations

Previously we interpreted circuits using the Boolean field $(\mathbb{F}_2, \cdot, \oplus)$ (note that $\{0,1\}^n = \mathbb{F}_2^n$).

Eg. $[\text{AND}] = \cdot$
 $[\text{XOR}] = \oplus$ "meaning" of a gate in the interpretation

We could instead interpret circuits using linear algebra by identifying the state of n bits with a unit vector $|x_1 \dots x_n\rangle \in \mathbb{F}_2^{2^n}$ and gates as linear operators from $\mathbb{F}_2^{2^n} \rightarrow \mathbb{F}_2^{2^n}$.

Ex. in the linear interpretation,

$$[\text{AND}] = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \text{ since } \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} |0\rangle = |1\rangle$$

$$[\text{XOR}] = \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

Note that $\begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} |01\rangle = \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$

$$\begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} |11\rangle = \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

Reversible computation

- Recall that physical processes are **reversible**
- The AND gate is not reversible, in the sense that we can't retrieve a & b from $a \cdot b$
e.g. if $a \cdot b = 0$, then what are a and b ?
 $\Rightarrow$ information is lost!

(Landauer's principle)

Erasing a single bit of energy dissipates at least $k_B T \ln 2$ of energy into the environment

(A reversible AND gate?)

The AND function can be computed "reversibly" by saving the inputs:



If we think of a physical process operating on a finite memory, this is **not** reversible because it may involve **overwriting** some other bit to store $a \cdot b$


(The Toffoli gate)

Tommaso Toffoli (1980) proposed the **Toffoli gate**



as a reversible AND gate completely conserving information (and hence reversible)

 
Using the Toffoli gate, the AND gate can be implemented with the aid of an **ancilla** (a bit in a known state)



(From irreversible to reversible)

we can make a classical circuit reversible by replacing each gate with a reversible analogue, given enough ancillas

Ex.

 


Thm.

A classical circuit running in space S and time T can be simulated by a reversible circuit running in space $O(S + T)$ and time $O(T)$

Pf.


Toffoli gate is universal:

 

Replacing each gate over a finite gate set takes constant time & space overhead $\square$

Uncomputation

 
- Reversible computation keeps allocating more and more space to store temporary values




- Need some way to **reclaim** space without **dissipating energy**

(The Bennett trick)

 After a computation is done, **copy** the output and **reverse** the computation to "uncompute" any temporary values.



 By intermittently uncomputing, space can be reduced at the expense of (potentially exponential) extra time



Thm. (Bennett 1989)

There exist pebbling strategies to simulate an irreversible computation with time T and space S reversibly with

- Time $O(T^{1+\epsilon})$ and space $O(S \log T)$
- Time $O(T)$ and space $O(ST^\epsilon)$

(Project idea: read Bennett's paper and implement or analyze his pebble games for a concrete class of circuits)